



# ECE2214

## Digital Logic Design

### L-23 More on counters



# Outline




- \* Synchronous counters with D flip-flops
- \* D-type FF counters with parallel loads
- \* Synchronous reset counters
- \* Other types of counters
  - BCD counters
  - Ring counters
  - Johnson counters


 
# Summary of previous lecture

- \* Registers are a set of  $n$  flip-flops used to store  $n$  bits of information
  - Shift registers enable shifting the content based on a clock signal




- \* Counters are special case of adders
  - Asynchronous and synchronous
  - Can be implemented with T, D and J-K FF




# Summary of previous lecture

- \* Asynchronous counters with T FF
  - Inputs  $T = 1$ , CLK are cascaded to allow consecutive counting

Up-counter

 

Down-counter

 



# Summary of previous lecture

## \* Synchronous counters with T FF

- All clocks are set together to obtain synchronization
- Inputs must to be combined to obtain counting sequence

$Q_3 Q_2 Q_1 Q_0$

1 1 1 1

1 1 1 0

1 1 0 1

1 1 0 0

1 0 1 1

1 0 1 0

1 0 0 1

...

...



0 1 0 0

0 0 1 1

0 0 1 0


0 0 0 1

0 0 0 0

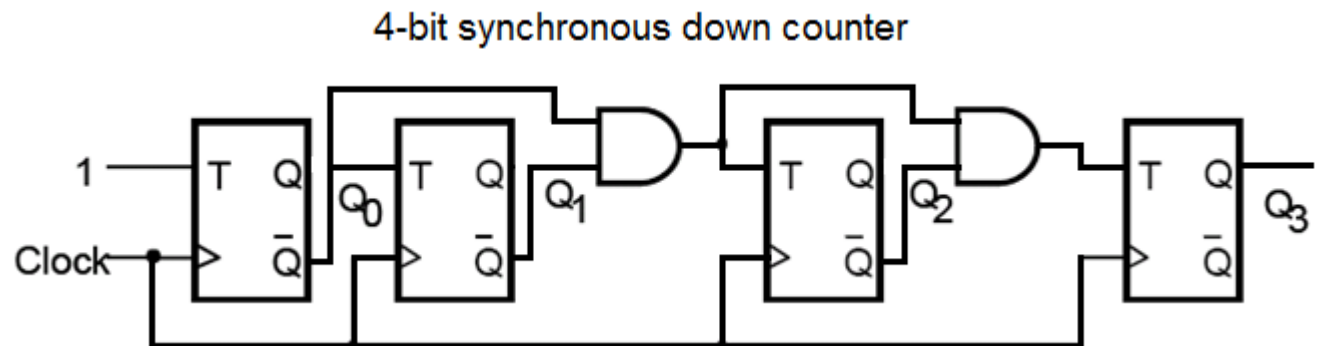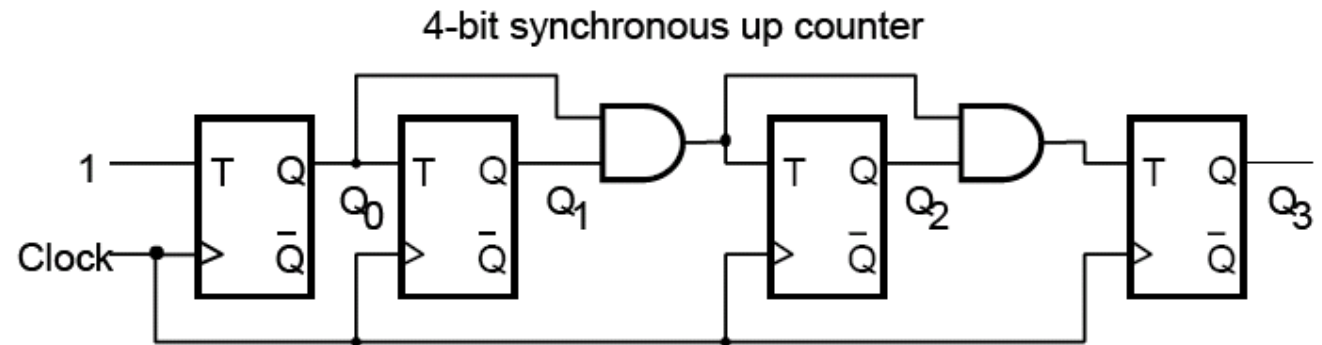



# Replacing T flip-flops by D flip-flops

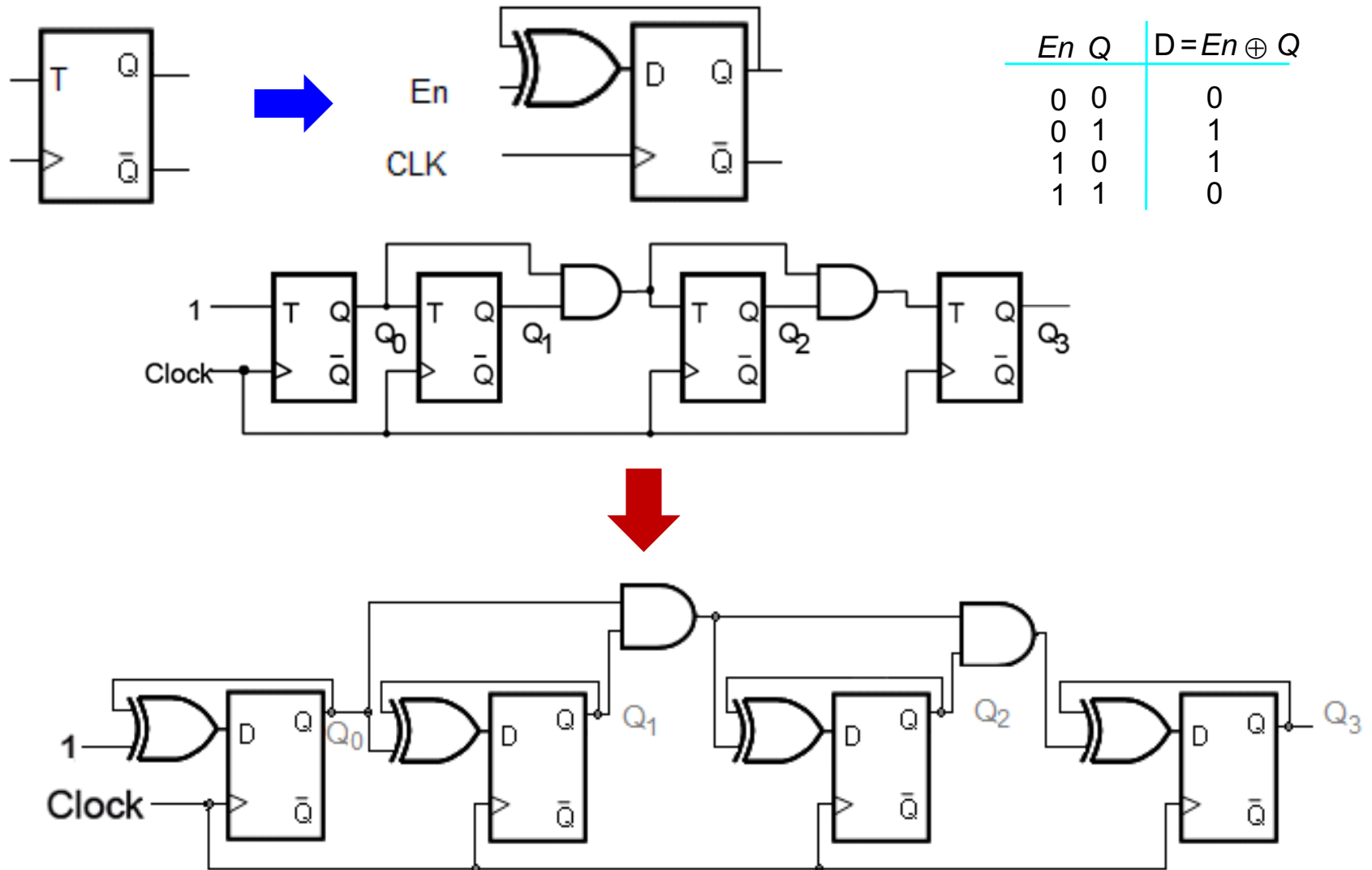




# Synchronous counters with D flip-flops

- \* D F-F need to set  $D=Q$  to hold/memorize the current state (when  $\text{CLK} \uparrow$ ,  $Q = D$ )
- \* Enable/disable properties must be implemented with logic
  - $E_N = 0$ , the counting is disabled (output of AND gate always 0 and  $Q$  is fed back to the  $D$  input holding the current state)
  - $E_N = 1$ , counting is enabled (output of AND gate will be  $Q$  from previous F-F and  $D$  will be toggle when previous  $Q_{N-1}$  differs from  $Q_N$ )

$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0

 

A four-bit counter with D flip-flops



# Generalization of synchronous counters implementation with D flip-flops

\* The equations that describe this implementation for an n bit counter are:

$$D_0 = Q_0 \oplus E_N$$

$$D_1 = Q_1 \oplus Q_0 E_N$$

$$D_2 = Q_2 \oplus Q_1 Q_0 E_N$$


$$D_3 = Q_3 \oplus Q_2 Q_1 Q_0 E_N$$

...

...

...
 
$$D_n = Q_n \oplus Q_{n-1} \cdot \dots \cdot Q_1 Q_0 E_N$$



A four-bit counter with D flip-flops





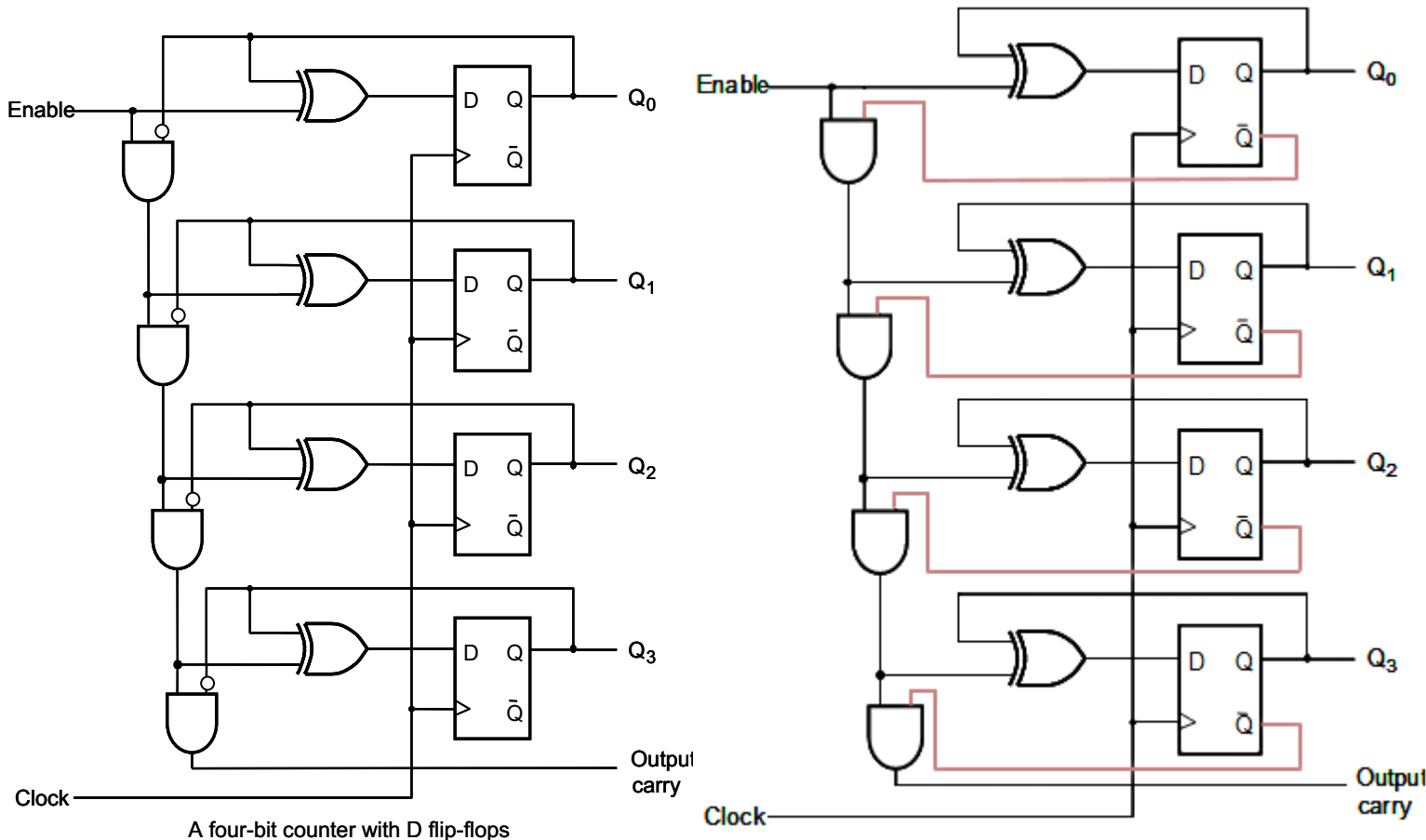
# Synchronous down counter with D flip-flops



- $Q_0$  complemented is fed back to the AND gate that enable other bits




$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0


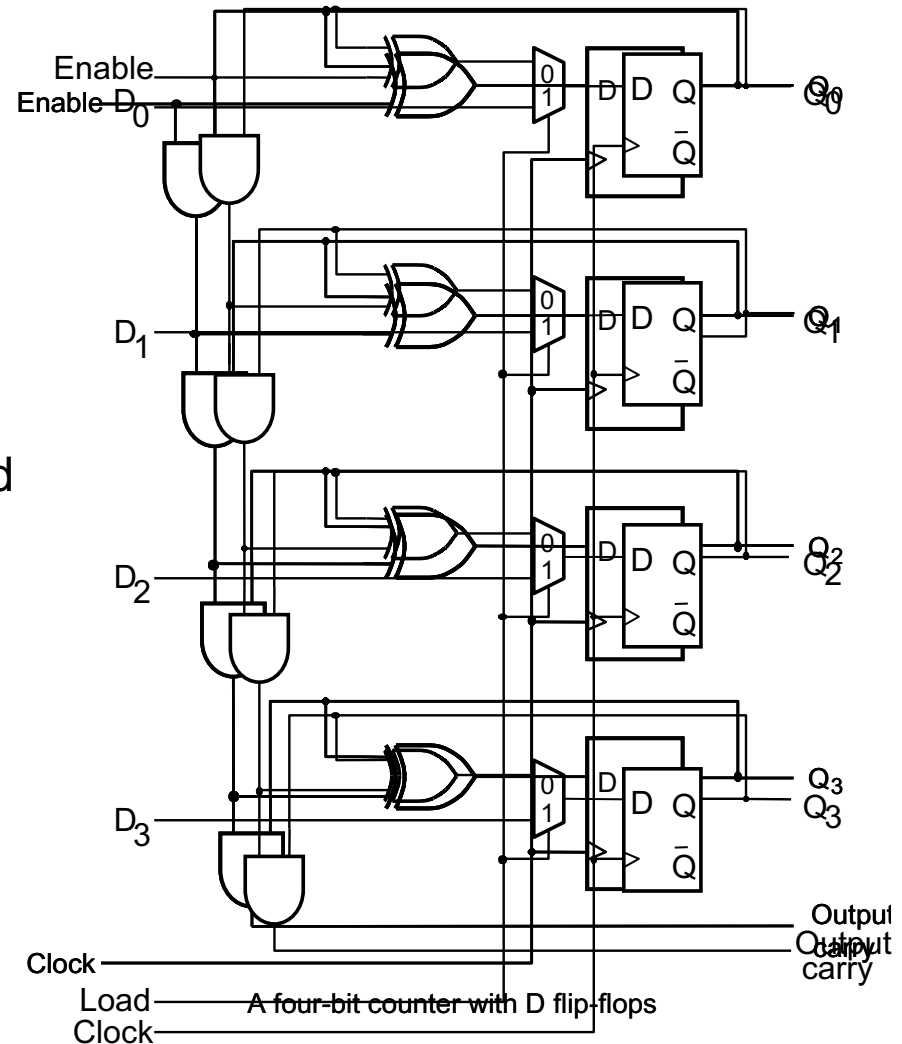
# Synchronous up counter with D flip-flops and parallel loads

- A multiplexer is added to select the external bit or cascade the previous stage
- External bit  $D_3D_2D_1D_0$  are loaded with Load = 1 and counts when load = 0
- Note that complexity of this implementation is remarkable compared to the same implementation using T F-Fs



A counter with parallel-load capability.



# Synchronous reset


- \* Synchronous reset is necessary when the application requires counting up to a number that is not a power of 2
- \* An N-bit binary counter is reset automatically after reaching the number  $2^N - 1$ 
  - A higher number will not fit in the available number of bits (N)
  - The output automatically are reset to 0
- \* Example
  - Suppose a 3-bit counter
    - ▶ CLK0 → 000
    - ▶ CLK1 → 001
    - ▶ CLK2 → 010
    - ▶ CLK3 → 011
    - ▶ CLK4 → 100
    - ▶ CLK5 → 101
    - ▶ CLK6 → 110
    - ▶ CLK7 → 111
    - ▶ CLK8 → 1000
  - \* **What if we don't want to count until the maximum value possible for N bits?**
    - Counting from 0 to 5 (module 6)
      - ▶ CLK0 → 000
      - ▶ CLK1 → 001
      - ▶ CLK2 → 010
      - ▶ CLK3 → 011
      - ▶ CLK4 → 100
      - ▶ CLK5 → 101
      - ▶ CLK6 → 000
      - ▶ CLK7 → 001
      - ▶ CLK8 → 010

\* **Need to add extra logic to reset the counter at CLK5**


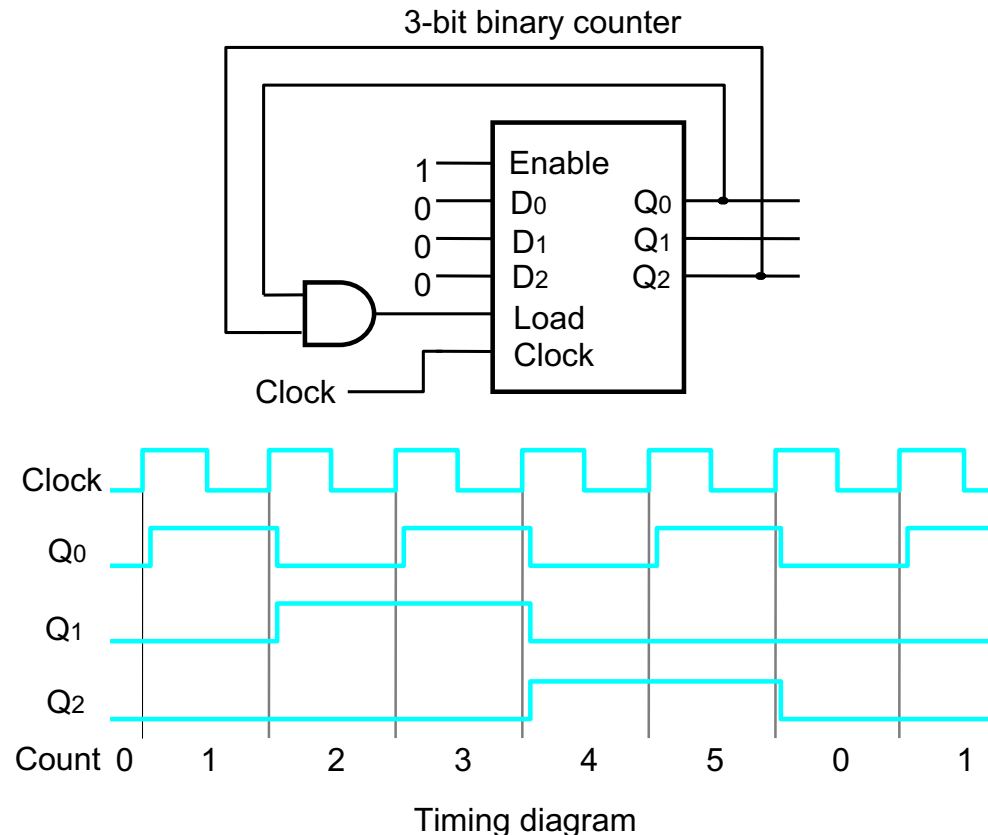
# Synchronous reset


- \* Suppose a counter Module 6 ( $C_6$ ) :
- \* The sequence of number are: 0,1,2,3,4,5,0,1 ...
- \* Need 3 bits to count from 0-5, but...
- \* Sequence 6 and 7 can't occur
- \* A logic circuit must be designed to:
  - Detect sequence 5 (101)
  - Set outputs to 000 with the next active CLK edge
- \* Reset of outputs can be generated
  - Using the load feature
  - Using the reset feature if F-F have synchronous reset input
- \* Notice from sequence 5
  - $D_2 = 1$  &  $D_0 = 1$  occurs only for 5
  - No other previous sequence has that unique combination




 
# Asynchronous reset

- \* Achieved when the signal that resets the counter is not clock synchronized
- \* Same example of the module 6 counter:
- \* Clear input is active low
- \* A NAND used to detect  $D_2 = 1$  &  $D_0 = 1$
- \* When the 5 occurs, then the CL inputs are activated...
- \* However, the number five will not be held for the whole clock cycle
  - Only during the time delay of NAND gate and the reset of the flip-flops
- \* Can be solved counting up to six and neglecting the glitch
  - NAND connected to  $D_2 = 1$  &  $D_1 = 1$



NOTE: This reset form is not always desirable since the delay introduced by the asynchronous reset could cause undesirable effects



# Design of up counters base N (non a power of 2)

## \* Synchronous reset for counters base N

1. Implement an up counter with base  $2^M$  where  $2^M$  next power of 2 after N
2. Determine the last state of the desired counting sequence (**N-1**)
3. Analyze a unique combination of bits of the **N-1** sequence
4. Design a logic that activate the parallel load synchronously or activate the synchronous reset

## \* Asynchronous reset for counters base N

1. Implement an up counter with base where  $2^M$  next power of 2 after N
2. Determine the last state of the desired counting sequence (**N**)
3. Analyze a unique combination of bits of the **N** sequence
4. Design a logic circuit that activate the asynchronous **clear /preset** inputs of flip-flops

## \* What if the counter counts downward?




# Design of synchronous down counters

- \* Similar to up counter but counter must be reset to the desired counting stage
- \* Best understood with an example
  - Design a 3-bit synchronous down counter with T FF that counts from **111** down to **011**

- \* Solution:

- The last counting sequence is 011
- $D_0 = 0$  is unique
- Activate  $P_r$  (active low)

 111  
110  
101  
100  
**011**  
010  
001  
000






# Design of asynchronous down counters

- ✧ Design a 3-bit asynchronous down counter with T FF that counts from **111** down to **011**

✧ Solution:

- The last counting sequence is 010
- $D_2 = 0$  &  $D_0 = 0$  are unique
- Activate Pr (active low) with an OR gate

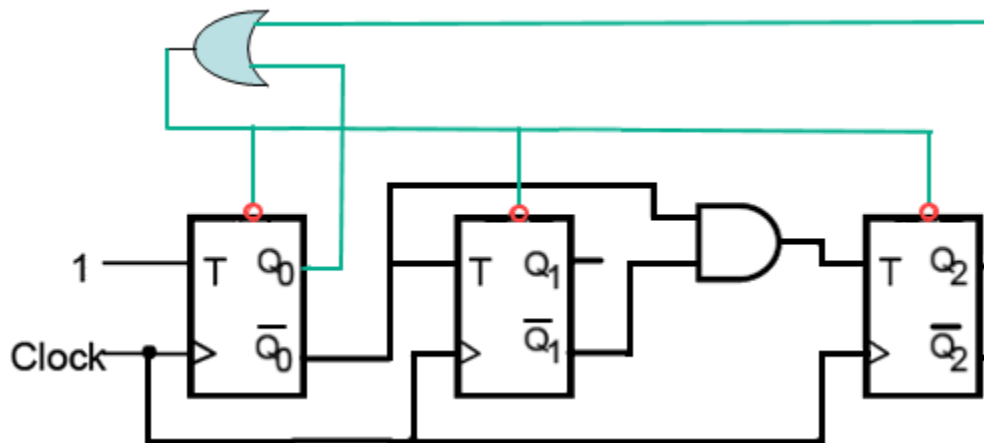111  
110  
101  
100  
011  
**010**  
001  
000







# Design of down counters base N (non a power of 2)

## \* Synchronous reset for counters base N

1. Implement a down counter with base  $2^M$  where  $2^M$  next power of 2 after N
2. Determine the last state of the desired counting sequence
3. Design the logic that activate the parallel load or reset/preset synchronously when  $2^M - N$  is reached
4. Activate the parallel load with the initial counting sequence (default  $2^M$ )

## \* Asynchronous reset for counters base N

1. Implement a down counter with base  $2^M$  where  $2^M$  next power of 2 after N
2. Determine last state of the desired counting sequence
3. Design the logic that activate the parallel load synchronously when  $2^M - (N+1)$  is reached
4. Activate the **preset/reset** inputs to set the initial counting sequence (default  $2^M$ )




# Other types of counters

- ✧ Counters of many different base or module can be implemented by resetting the counting sequence when the desired number is met
- ✧ One example is a 2-bit BCD counter

- ✧ **BCD counter**

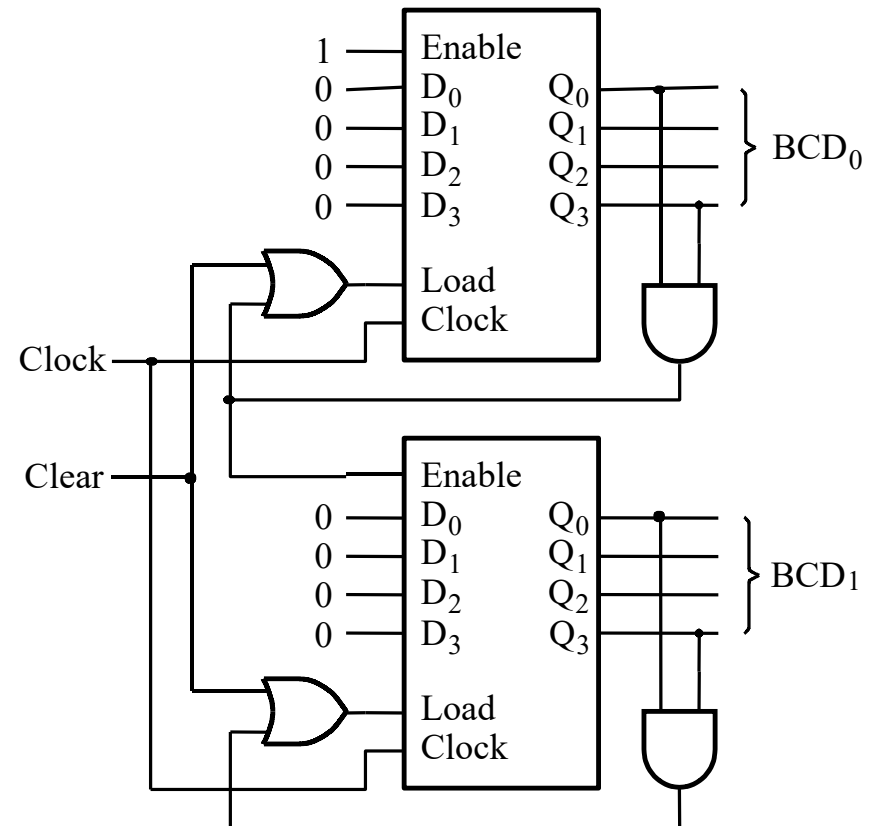- A binary-coded-decimal counter is based on a modulus 10 counter
  - Last sequence is **1001**
  - An AND gate is used to load 0000
  - Same signal activate the second digit
  - An external clear was added
- ✧ BCD counter is widely used to perform arithmetic operation in decimal system and provide the number to display in a 7-segment format






# Other types of counters
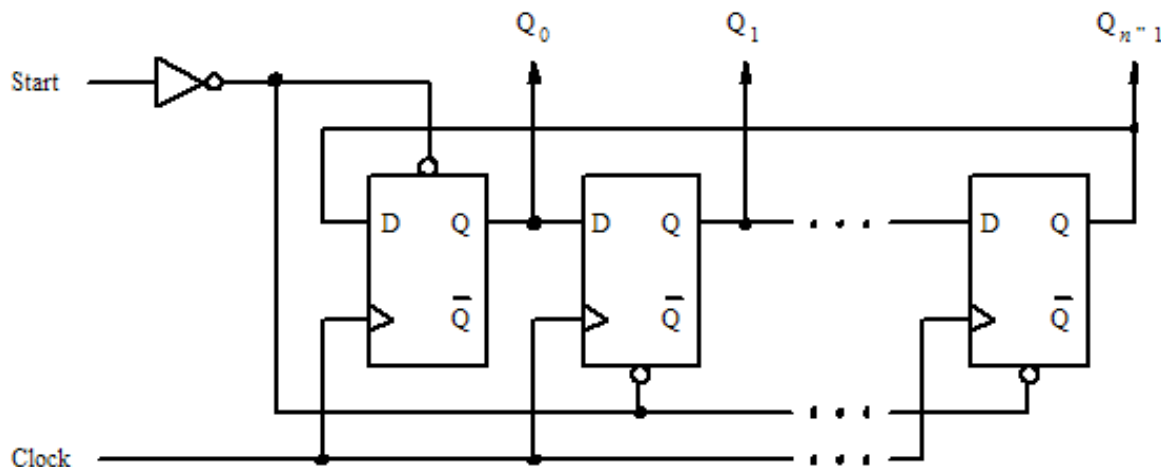
## \* Ring counters

- Ring counters are special type of counter that the output is not a binary number
- Activate only one output in each clock cycle
- The output of the last bit is fed back to the input
- The output pattern is repeated after the last output is activated creating a type of ring
- The best implementation of a ring counter is by injecting a '1' to a shift register and shifting it to one of the sides






# Other types of counters
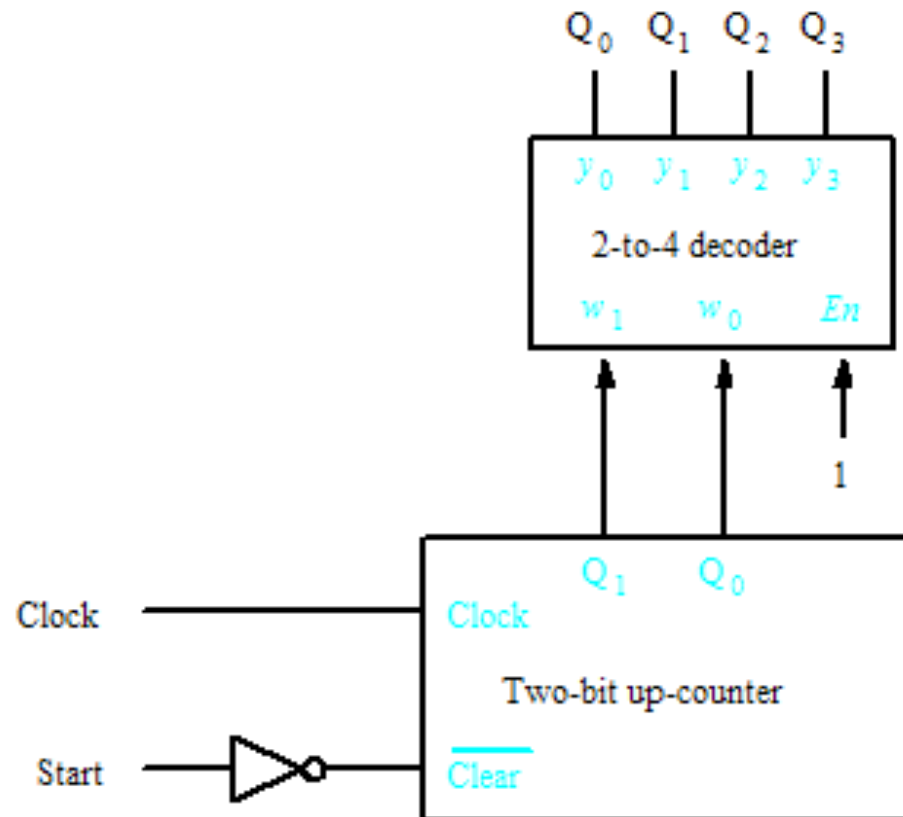
## \* Ring counter

- Same counter can be implemented by combining a 2-bit binary counter and a decoder
- Example:






# Other types of counters
 
## \* Johnson counters

- This is a counter that is obtained from a slight modification to the ring counter
- Feeds back the complemented output of the last digit instead of  $Q$
- This makes that the pattern:



Example:

0000  
0001  
0011  
0111  
1111  
1110  
1100  
1000  
0000  
0001  
0011  
0111  
1111  
...



# Summary



- \* Synchronous counters with D flip-flops
- \* D-type FF counters with parallel loads
- \* Synchronous reset counters
- \* Design of an arbitrary base down and up counters
- \* Other types of counters : BCD, ring counters and Johnson counters
- \* Reference
  - Fundamentals of Digital Logic with VHDL Design 3/e, Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2009. Chapter 7, pp. 409-418
  - Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 7, pp. 710-727
- \* Recommended exercises from the book
  - 1. Problems of pp. 473 of textbook
    - \* 7.23 - 7.31