



ECE 2214

Digital Logic Design

L-17 Design of arithmetic using CAD tools

Fall 2022



Outline



- ✧ Schematic description of arithmetic logic circuits
- ✧ VHDL description of arithmetic logic circuits
 - Modules and packages
 - Number representations in VHDL
 - Arithmetic operators in VHDL
- ✧ Arithmetic assignment statements in VHDL



Summary of previous lecture

- * Learned multiplication and division of binary numbers
- * Fractional representation
 - Fix point representation

$$B = b_{n-1} b_{n-2} \dots b_0 \bullet b_{-1} b_{-2} \dots b_{-k}$$

- Floating number representation

$$\text{Value}_{10} = \pm 1.M * R^{E-\text{bias}}$$



Binary-coded-decimal representation (BCD)



- * Use four bits to encode each decimal digits. Each digit is encoded using unsigned binary representation as:

Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Note:

- * Decimal digit (0...9) → only need 4 bits
- * Only the first 10 of the 16 possible numbers obtained with 4 bits are used, the rest can't occur in BCD
- * Benefit: provide a format that is easy to display
 - Not commonly used in current computers
- * The arithmetic operation of BCD can be complicated
 - Any arithmetic result $>(9)_{10}$ must keep the excess magnitude of 9 and carry one to the next digit

- * Example 6: Convert the following BCD number into binary

$$\begin{array}{ccc} 9 & 3 & 4 \\ 1001 & 0011 & 0100 \end{array}$$



ASCII Character code



- * This is the standard code for storing text characters
 - Each letter and special character has a unique code
- * It uses 7 bits to represent each character (127 in total)
- * Example 7: Describe the relationship between decimal, ASCII and binary code for numbers from 0..9

$$(0)_{10} = 30_{\text{ASCII}} = (0110000)_2$$

$$(1)_{10} = 31_{\text{ASCII}} = (0110001)_2$$

$$(2)_{10} = 32_{\text{ASCII}} = (0110010)_2$$

$$(3)_{10} = 33_{\text{ASCII}} = (0110011)_2$$

$$(4)_{10} = 34_{\text{ASCII}} = (0110100)_2$$

$$(5)_{10} = 35_{\text{ASCII}} = (0110101)_2$$

$$(6)_{10} = 36_{\text{ASCII}} = (0110110)_2$$

$$(7)_{10} = 37_{\text{ASCII}} = (0110111)_2$$

$$(8)_{10} = 38_{\text{ASCII}} = (0111000)_2$$

$$(9)_{10} = 39_{\text{ASCII}} = (0111001)_2$$

See 5.4 pp. 302 of the textbook for a full list



Design of arithmetics using CAD tools




- * There are two approaches designing arithmetic circuits
 1. Schematic description
 - ▶ Involve providing the schematic that contains the logic gates performing the arithmetic
 2. Used HDL languages (VHDL)
 - ▶ Involve providing scripts that describe operation of the circuit that perform the arithmetic operation



Schematic description of arithmetic circuits



 
- ✧ Higher level arithmetic has to be designed and wired graphically using hierarchical file structures
- ✧ Example: To create an n -bit adder you could design a one-bit full-adder module and connect n instances of the that module



- ✧ More cumbersome, especially when the number of bits is high but...
- ✧ You can use standard modules available in Quartus library for most of the basic arithmetic operations
 - Some modules are technology dependent
 - Others are generic for any type of chip




Use of the schematic arithmetic library

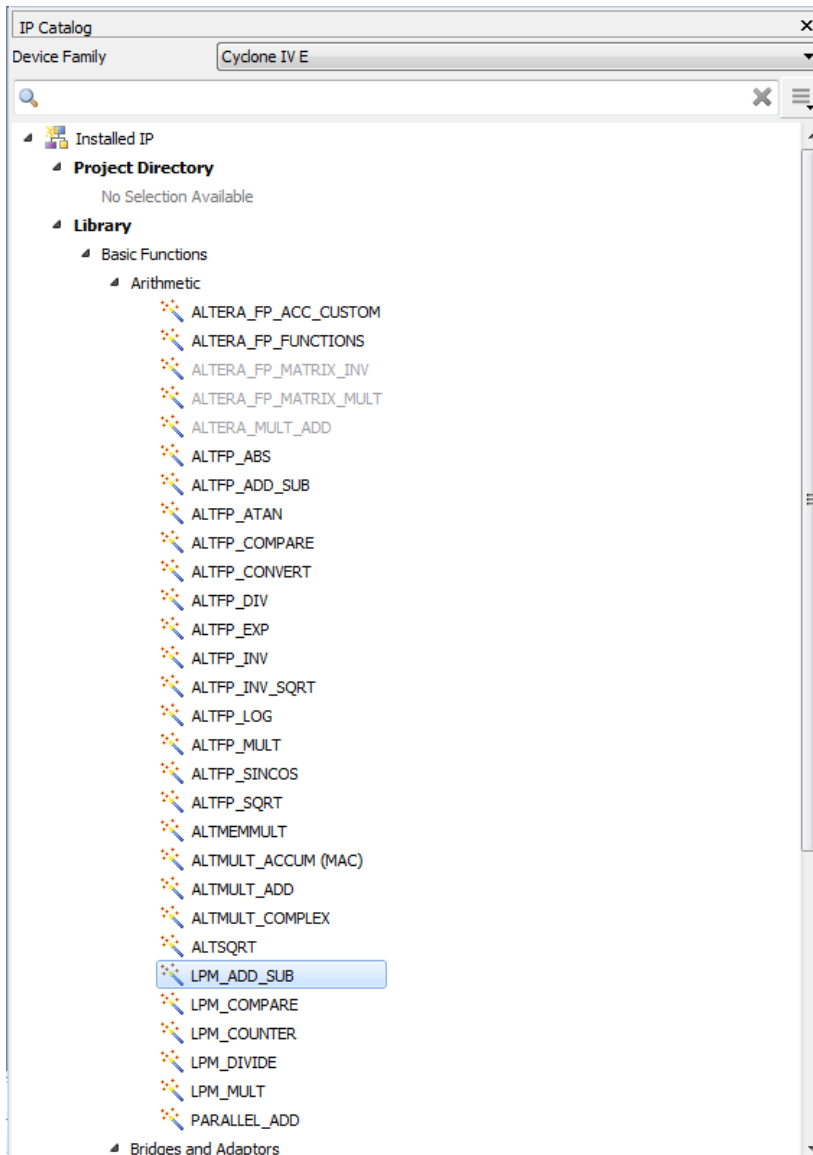

* Arithmetic library available from the menu of Quartus II

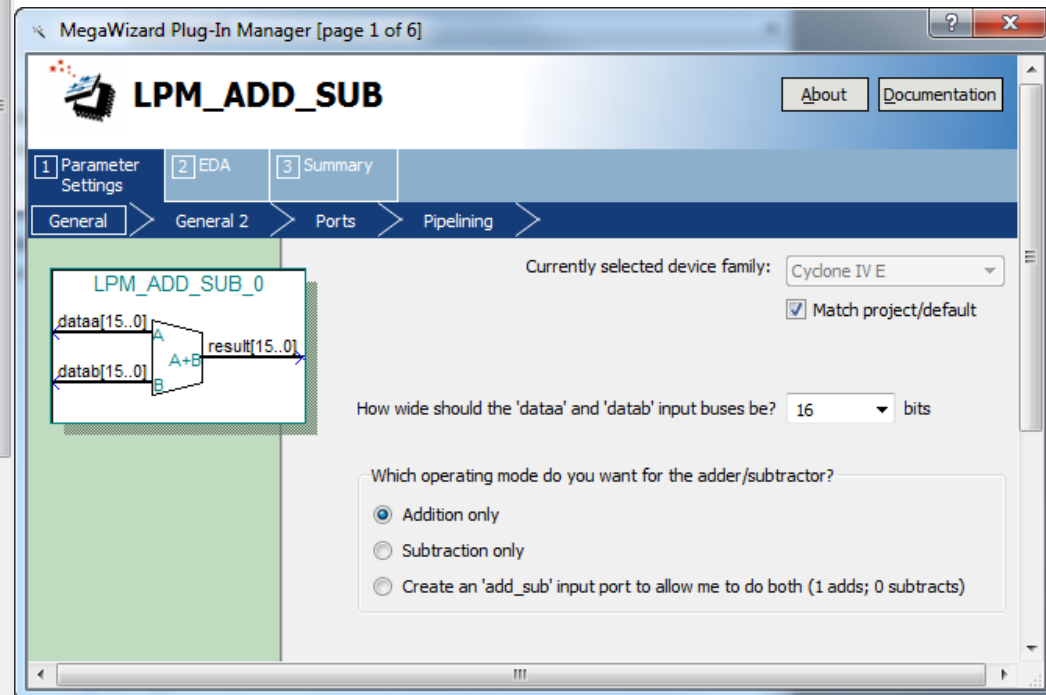- \Tools\IP Catalog
- Several modules available
 - # of bits configurable!





LPM library arithmetic library

- * Can generate more than one format

MegaWizard Plug-In Manager [page 6 of 6]

LPM_ADD_SUB [About] [Documentation]

1 Parameter Settings 2 EDA 3 Summary

LPM_ADD_SUB_0

dataa[15..0] A result[15..0] A+B
datab[15..0] B

Resource Usage
16 lut

Turn on the files you wish to generate. A gray checkmark indicates a file that is automatically generated, and a green checkmark indicates an optional file. Click Finish to generate the selected files. The state of each checkbox is maintained in subsequent MegaWizard Plug-In Manager sessions.

The MegaWizard Plug-In Manager creates the selected files in the following directory:
C:\altera\14.0\


File	Description
<input checked="" type="checkbox"/> LPM_ADD_SUB_0.vhd	Variation file
<input type="checkbox"/> LPM_ADD_SUB_0.inc	AHDL Include file
<input type="checkbox"/> LPM_ADD_SUB_0.cmp	VHDL component declaration file
<input checked="" type="checkbox"/> LPM_ADD_SUB_0.bsf	Quartus II symbol file
<input type="checkbox"/> LPM_ADD_SUB_0_inst.vhd	Instantiation template file

[Cancel] [Back] [Next] [Finish]



Use of the schematic arithmetic library

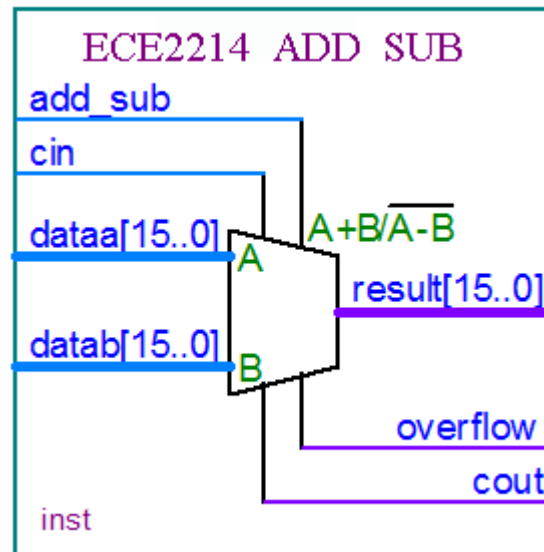
- * Module generated with the IP Catalog
 - 16-bits adder
 - Carry-out
 - Overflow detection





Use of the schematic arithmetic library

 
- * IP Catalog library has other modules
- * i.e. Multiplication
 - 8-bits multiplier
 - ▶ Two 8-bit input numbers
 - ▶ One 16 bit output number





Use of the schematic arithmetic library

 - * IP Catalog library has other modules
- * i.e. division
 - Unsigned number divider
 - ▶ Two 8-bit input numbers
 - ▶ One 8-bit quotient output
 - ▶ One 8-bit remainder output





Arithmetic with HDL languages




- * Involve the development of scripts that perform the arithmetic operations
- * Scripts have to follow certain structure given by the language used
 - VHDL has a general script structure based on Entity-Architecture
 - i.e. Similar to the adder generated before but with only 1 bit

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY fulladd_L18_Slide11 IS  
  PORT(Cin , x, y : IN    STD_LOGIC;  
        s, Cout   : OUT   STD_LOGIC);  
END;  
  
ARCHITECTURE logicFunc OF fulladd_L18_Slide11 IS  
  BEGIN  
    s <= (x XOR y) XOR Cin ;  
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y);  
  END LogicFunc;
```

$$S_i = x_i \oplus y_i \oplus c_i$$
 
$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$



- * N-bit carry adder is implemented instantiating this module n-times



Arithmetic with VHDL language

Direct implementation with basic sentences



✱ Example of a 4-bit ripple carry adder

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY adder4_L18_slide12 IS
    PORT (
        Cin : IN STD_LOGIC ;
        x3, x2, x1, x0 : IN STD_LOGIC ;
        y3, y2, y1, y0 : IN STD_LOGIC ;
        s3, s2, s1, s0 : OUT STD_LOGIC := '0' ;
        Cout : OUT STD_LOGIC ) ;
```

```
END adder4_L18_slide12 ;
```

```
ARCHITECTURE Structure OF adder4_L18_slide12 IS
```

```
    SIGNAL c1, c2, c3 : STD_LOGIC ;
```

```
    COMPONENT fulladd_L18_Slide11
```

```
        PORT(Cin , x, y : IN STD_LOGIC;
              s, Cout : OUT STD_LOGIC);
```

```
    END COMPONENT ;
```

```
BEGIN
```


```
    stage0: fulladd_L18_Slide11 PORT MAP ( Cin, x0, y0, s0, c1 ) ;
```

```
    stage1: fulladd_L18_Slide11 PORT MAP ( c1, x1, y1, s1, c2 ) ;
```

```
    stage2: fulladd_L18_Slide11 PORT MAP ( c2, x2, y2, s2, c3 ) ;
```

```
    stage3: fulladd_L18_Slide11 PORT MAP (c3, x3, y3, s3, Cout) ;
```

```
END Structure ;
```

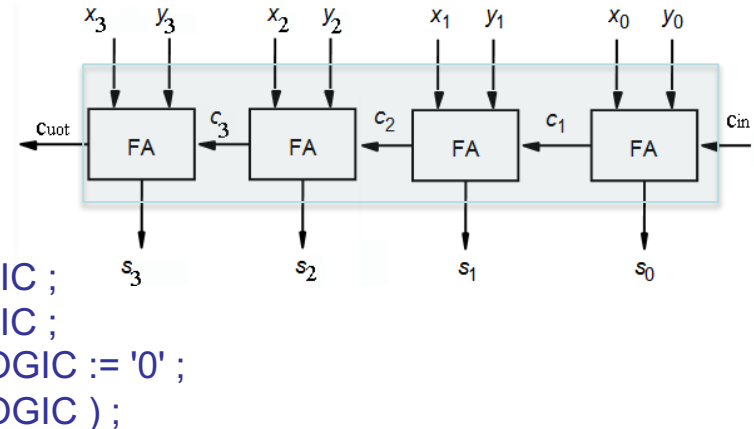

A file must be saved with the same name:
Fulladd_L18_Slide11.vhd

✱ Component structure used to instantiate fulladd module 4 times



Arithmetic with VHDL language

Direct implementation with basic sentences

* Observations

- Four bits are declared for the inputs **x** and **y** and for the output **s**
- A separate bit is declared for the **Cout** and **Cin**
- The code that perform the full adder “fulladd” is declared as a COMPONENT
- The typical declaration of a component is:

```
COMPONENT name  
    PORT ( in1, in2, ... inN    : IN DataType ;  
          out1, out2, ... outN: OUT DataType );  
END COMPONENT ;
```

- Name of component function must match the filename containing it
- Internal variables or signals can be declared to store temporary results
 - ▶ Such as c1, c2 and c3
- The declaration for the internal variables is:

```
SIGNAL vname1, vname2 ... vnameN : DataType ;
```



Arithmetic with VHDL language

Direct implementation with basic sentences

- * Same function can be implemented with several approaches
- * i.e. The same previous example can be written with an alternative style
 - Use VHDL package sentence instead of the component used before
 - A library style

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
PACKAGE fulladd_package IS  
    COMPONENT fulladd_L18_Slide11  
        PORT ( Cin, x, y      : IN STD_LOGIC ;  
              s, Cout       : OUT STD_LOGIC );  
    END COMPONENT ;  
END fulladd_package ;
```

The file fulladd_package.vhd must exist. It can have the implementation of fulladd_L18_Slide11 or use it from the separate file



HDL languages

Direct implementation with basic sentences

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE work.fulladd_package.all;
```

```
ENTITY fulladd_L18_Slide15 IS
```

```
    PORT (    Cin           : IN          STD_LOGIC ;  
             x3, x2, x1, x0 : IN          STD_LOGIC ;  
             y3, y2, y1, y0 : IN          STD_LOGIC ;  
             s3, s2, s1, s0 : OUT         STD_LOGIC ;  
             Cout           : OUT         STD_LOGIC ) ;
```

```
END fulladd_L18_Slide15 ;
```


```
ARCHITECTURE Structure OF fulladd_L18_Slide15 IS
```

```
    SIGNAL c1, c2, c3 : STD_LOGIC ;
```

```
BEGIN
```

```
    stage0: fulladd_L18_Slide11 PORT MAP ( Cin, x0, y0, s0, c1 ) ;  
    stage1: fulladd_L18_Slide11 PORT MAP ( c1, x1, y1, s1, c2 ) ;  
    stage2: fulladd_L18_Slide11 PORT MAP ( c2, x2, y2, s2, c3 ) ;  
    stage3: fulladd_L18_Slide11 PORT MAP ( c3, x3, y3, s3, Cout ) ;
```

```
END Structure ;
```

 



HDL languages

Direct implementation with basic sentences



- ✧ The package is a more organized style
 - Structure the 1-bit adder as a package
 - The package is saved as a library (`work.fulladd_package.all` in this case)
 - The library can be stored in a separate file in the same work directory

- The 4-bit adder script instantiate the 1-bit adder 4 times

Both code styles do the same operation
You can use the one that you prefer!



Number representation in VHDL

Basic number formats

- * VHDL has different data objects to represent individual logic signals or wires
- * A signal has to be declared with type associated in the following format:

SIGNAL signal_name : type_name;

- * The type_name determines the values that the signal can have and ... its use in VHDL
- * The most common signal types are:
 - BIT
 - BIT_VECTOR
 - STD_LOGIC
 - STD_LOGIC_VECTOR
 - INTEGER (SIGNED or UNSIGNED)
 - BOOLEAN
 - ENUMERATION



Number representations in VHDL

Basic number formats

- * **BIT or BIT_VECTOR:** Are predefined VHDL types to define the number of bits of a signal

BIT: Represent one bit and can have value '0' or '1'

BIT_VECTOR: Represent a linear array of BITS

Use: "TO" or "DOWNTO" specify the bit range

- * Example:

```
SIGNAL X      : BIT;  
SIGNAL X      : BIT_VECTOR (1 TO 4);  
SIGNAL X      : BIT_VECTOR (7 DOWNTO 0);
```

Note:

- TO indicate the direction from MSB (1) to LSB (4)
- DOWNTO indicate the direction from MSB (7) to LSB(0)
- Special care has to be taken in this definition since the interpretation of the result depends on the bit definition



Number representations in VHDL

Basic number formats

- * **STD_LOGIC or STD_LOGIC_VECTOR:** Added to VHDL by IEEE 1164 standard library
 - Provides more flexibility than the BIT type
 - Store standard logic data such as bits and vectors
- * Requires the term “USE ieee.std_logic_signed” for signed numbers and ... the term “USE ieee.std_logic_unsigned” for unsigned numbers in the script heading

STD_LOGIC: Can hold different values ‘0’, ‘1’, ‘Z’(high impedance), ‘-‘ (don’t care)

STD_LOGIC_VECTOR: Represent a linear array of STD_LOGIC

Use ‘TO’ or DOWNTO to specify the limits of the bits that the object holds

- * Example:

```
SIGNAL X    : STD_LOGIC;  
SIGNAL X    : STD_LOGIC_VECTOR (1 TO 4);  
SIGNAL X    : STD_LOGIC_VECTOR (7 DOWNTO 0);
```



Number representations in VHDL

Basic number formats

- * **INTEGER:** It is part of the standard VHDL code to represent signed numbers
 - Is designed to be use with arithmetic operators
- * It has 32 bits by default and can represent number from $-(2^{31}-1)$ to $(2^{31}-1)$.
- * Integer with fewer bits can be declared using the keyword RANGE

INTEGER: Represent a 32-bit integer type

INTEGER RANGE $-L_1$ TO L_2

**Represent an integer number with fewer bits than 32
determined by L_1 and L_2**

Example:

```
SIGNAL X : INTEGER;
```

```
SIGNAL X : INTEGER RANGE -127 TO 127; (8 Bits)
```

- * **BOOLEAN:** Only have TRUE ('1') or FALSE ('0') values
- * Example:

```
SIGNAL X : Boolean;
```



Number representations in VHDL

Basic number formats

- * **ENUMERATION:** Signal can only have one of the user defined values

- Signal is declared as the user defined type

```
TYPE enumeration_type_name IS (name1, name2, ... nameN);
```

```
SIGNAL X : enumeration_type_name;
```

Example:

```
TYPE State_Type IS (stateA, stateB, stateC);
```

```
SIGNAL y : State_Type;
```

- * **Array:** used with custom-defined data type specified before

```
TYPE array_type_name IS ARRAY (index_range) OF element_type;
```

```
SIGNAL array_name : array_type_name [:= initial_values];
```

Example:

```
TYPE Int4 IS ARRAY (1 to 4) OF integer;
```

```
SIGNAL x : Int4;
```




Arithmetic operators in VHDL

Operators & precedence

- * A number of operators are defined in VHDL to perform arithmetic operations (**requires the use of IEEE library**)
- * The arithmetic operators are highlighted

P
r
e
c
e
d
e
n
c
e

 

1. Binary logical operators: **AND, OR, NAND, NOR, XOR, XNOR**
2. Relational operators: **=, /=, <, <=, >, >=**
3. Shift operators: **sll, srl, sla, sra, rol, ror**
4. Adding operators: **+, -, & (concatenation)**
5. Unary sign operators: **+, -**,
6. Multiplying operators: ***, /, mod, rem**
7. Miscellaneous operators: **not abs ****

Note:

- Operators of the same precedence will be evaluated from left to right.
- Bracket will change the precedence of operators.

X AND Y OR Z AND M is not **XY + ZM** → **(X AND Y) OR (Z AND M)**



Statements for arithmetic assignment in VHDL

Assignment of variables

The assignment in VHDL is accomplished as follow:

`signal_name <= expression;`

i.e If the following signals are defined

`SIGNAL X,Y,S : STD_LOGIC_VECTOR_UNSIGNED (15 DOWNT0 0)`

Addition operation statement : `S <= X + Y;` (16-bit adder)

Multiplication operation statement : `S <= X * Y;` (16-bit multiplier)


A special and very important case is assigning constants to variables. In VHDL you can assign values to bits separately or in groups:

`signal_name <= 'C';` → simple assignment of constant C to signal_name
i.e. `X <= '1';`

`signal_name <= "C0C1 C2 ... CN-1CN";` Multiple assignment of constants C to signal_name. i.e. `X <= "1001"`.




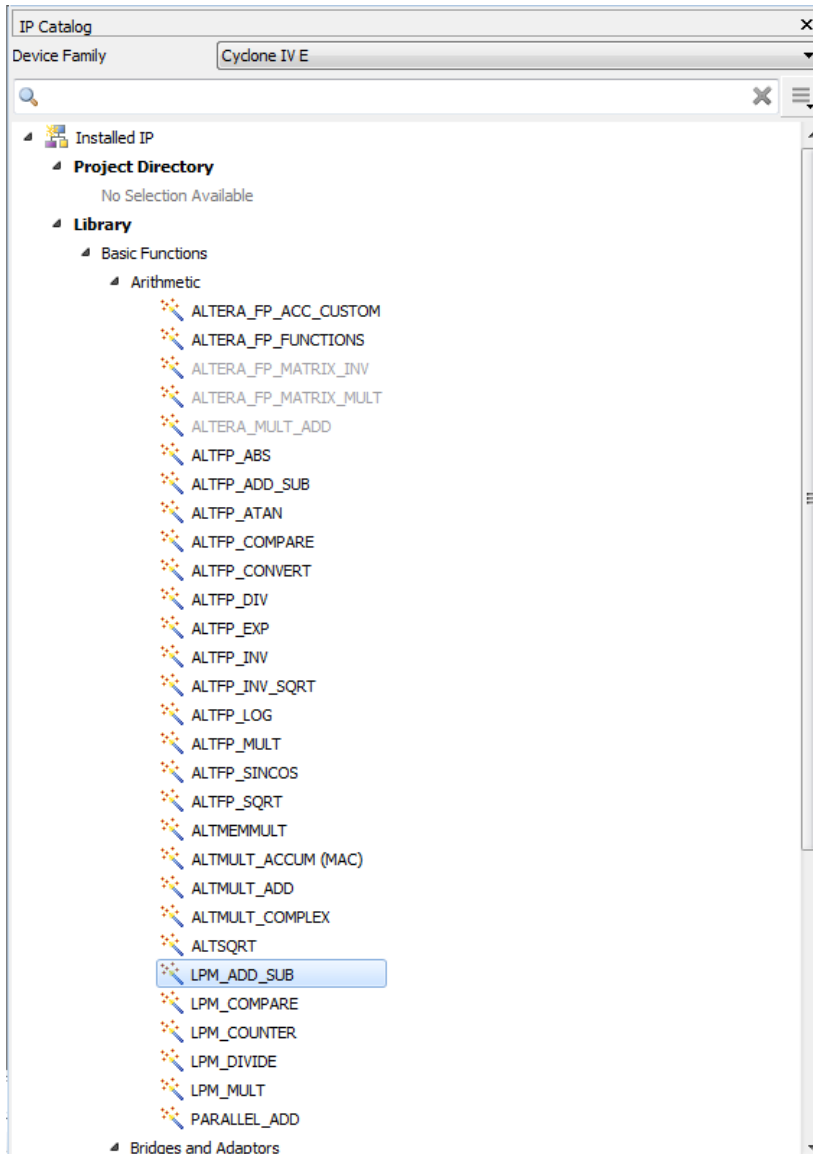Use of the VHDL pre-built arithmetic library



* Similar to the schematic arithmetic library, you can generate arithmetic templates

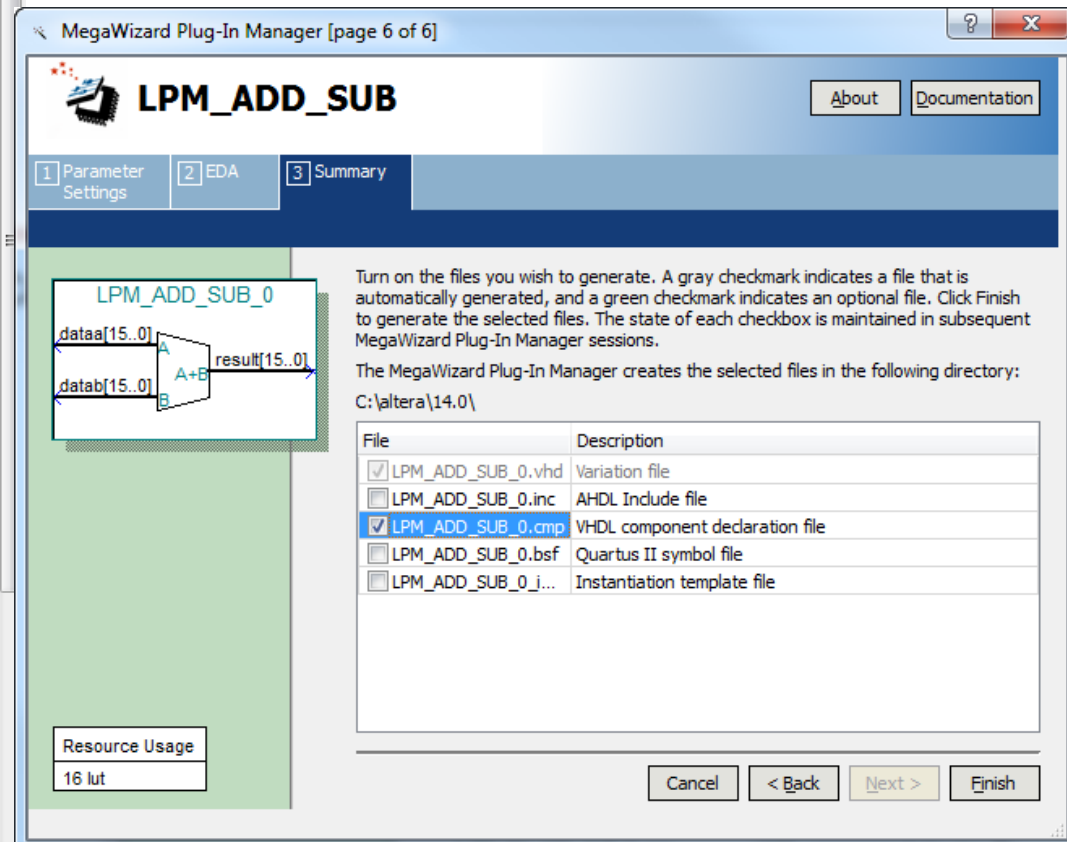- \Tools\IP Catalog
- Several configurable modules





Arithmetic with VHDL: QII LPM library



* Files generated:

- L4_4_Bit_Adder.qip
- L4_4_Bit_Adder.vhd (fraction of the code below)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY lpm;
USE lpm.all;

ENTITY L4_4_Bit_Adder IS
  PORT
  (
    dataa      : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    datab      : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    cout        : OUT STD_LOGIC ;
    overflow     : OUT STD_LOGIC ;
    result      : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)
  );
END L4_4_Bit_Adder;

ARCHITECTURE SYN OF l4_4_bit_adder IS

  SIGNAL sub_wire0 : STD_LOGIC ;
  SIGNAL sub_wire1 : STD_LOGIC ;
  SIGNAL sub_wire2 : STD_LOGIC_VECTOR (3 DOWNTO 0);
```

- * Use component to reuse the VHDL code generated
- * Similarly you can generate multiplier, divider circuits




Arithmetic with VHDL: QII LPM library



* 4-bit adder implementation

```
1  -- Quartus II VHDL- Unsigned 4-bit carry adder
2  -- ECE2215 L4
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  entity L4_4_BIT_ADDER is
8  port (
9      a          : in STD_LOGIC_VECTOR (3 downto 0);
10     b          : in STD_LOGIC_VECTOR (3 downto 0);
11     carryout    : out STD_LOGIC;
12     overflow    : out STD_LOGIC;
13     sum         : out STD_LOGIC_VECTOR (3 downto 0)
14 );
15 end entity;
16
17 architecture rtl of L4_4_BIT_ADDER is
18     COMPONENT FOUR_BIT_ADDER IS
19         PORT
20         (
21             dataa      : IN STD_LOGIC_VECTOR (3 DOWNT0 0);
22             datab      : IN STD_LOGIC_VECTOR (3 DOWNT0 0);
23             cout       : OUT STD_LOGIC ;
24             overflow   : OUT STD_LOGIC ;
25             result     : OUT STD_LOGIC_VECTOR (3 DOWNT0 0)
26         );
27     END COMPONENT;
28
29 begin
30
31     I1: FOUR_BIT_ADDER PORT MAP (a, b,carryout,overflow, sum);
32
33 end rtl;
```

Simulation results

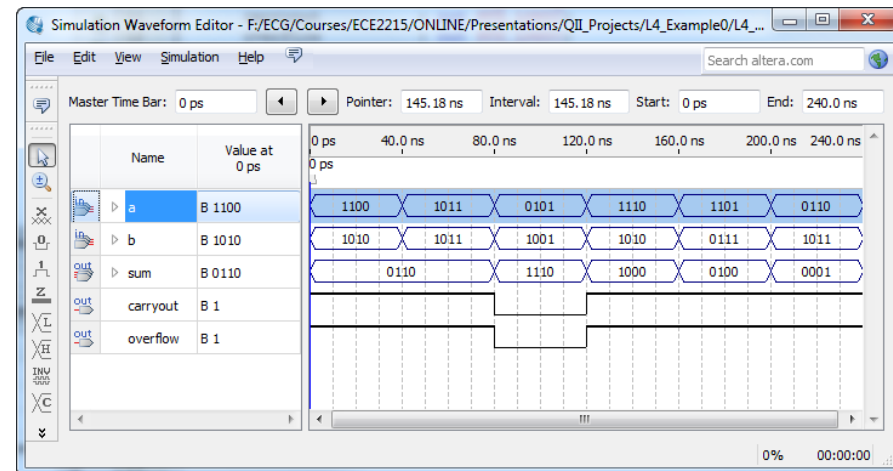



Arithmetic with VHDL

IEEE Numeric library



- * This is the easiest approach
- * Must include the library in your design as “use ieee.numeric_std.all;”
- * Includes operators for signed and unsigned arithmetic
 - Automatically select the right operation based on type of operands
 - Supported operators: ‘+’, ‘-’, ‘*’, ‘/’, ‘rem’, ‘mod’, ‘**’, ‘abs’
 - Other comparison and converting functions as seen in:
http://www.csee.umbc.edu/portal/help/VHDL/packages/numeric_std.vhd
 - Also support shifting operations basic gates with signed/unsigned types




Arithmetic with VHDL

IEEE Numeric library



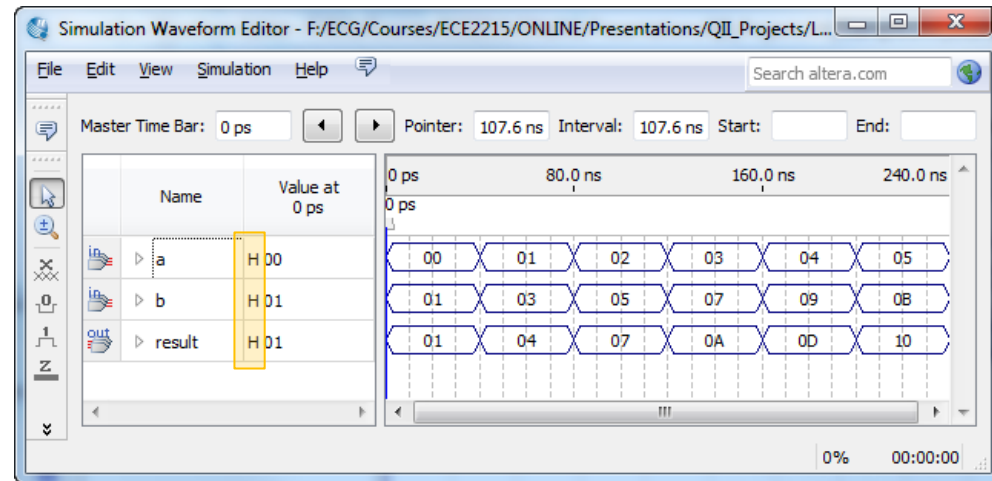* Example 1: 8-bit unsigned adder

```
1  -- L4 Example 1- Eight-bit unsigned adder
2  -- ECG 2016
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use ieee.numeric_std.all;
7
8  entity L4_8bit_unsigned_adder is
9      generic
10         (
11             DATA_WIDTH : natural := 8
12         );
13     port
14     (
15         a      : in unsigned ((DATA_WIDTH-1) downto 0);
16         b      : in unsigned ((DATA_WIDTH-1) downto 0);
17         result : out unsigned ((DATA_WIDTH-1) downto 0)
18     );
19 end entity;
20
21 architecture rtl of L4_8bit_unsigned_adder is
22 begin
23
24     result <= a + b;
25
26 end rtl;
27
28
```



* All signed numbers are represented in hexadecimal as indicated by the H besides the variable name



Summary

- * We introduced the design of arithmetic using CAD tools.
- * There are two options:
 - Graphical description of arithmetic logic circuits
 - VHDL description of arithmetic logic circuits
- * Both cases have predefined modules in the arithmetic library
 - \Tools\Mega Wizard Plug-in Manager
- * We introduced all necessary information regarding VHDL to design arithmetic statements that work with signed and unsigned number representation

- * References
 - Fundamentals of Digital Logic with VHDL Design 2nd Edition Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005. Chapter 5, pp. 278-289
 - Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 5, pp. 256-289