



# ECE2215

## Digital Logic Design Lab

### Lab 9- Tutorial on Arithmetic with VHDL

*Dr. Eduardo Castillo-Guerra*

1

1



## Outline

- \* Arithmetic operators in VHDL
- \* Arithmetic with QII libraries
  - Signed and floating-point numbers
- \* Arithmetic with Numeric Standard Library
  - Signed and unsigned numbers

*Dr. Eduardo Castillo-Guerra*

2

2



## Design of arithmetic using CAD tools



- \* There are two approaches designing arithmetic circuits
  1. Schematic description
    - ▶ Involve providing the schematic that contains the logic gates performing the arithmetic
    - ▶ Not attractive for complex circuits
  2. Used HDL languages (VHDL)
    - ▶ Involve providing scripts that describe operation of the circuit that perform the arithmetic operation
    - ▶ Three alternatives
      1. Use default sentences in VHDL to implement the arithmetic
      2. Use QII libraries (i.e. LPM library)
      3. Use IEEE standard libraries (i.e. ieee.numeric\_std library)

Dr. Eduardo Castillo-Guerra

3


3


 
## Schematic description of arithmetic circuits



- \* Higher level arithmetic has to be designed and wired graphically using hierarchical file structures
- \* Example: To create an n-bit adder you could design a one-bit full-adder module and connect n instances of the that module



- \* More cumbersome, especially when the number of bits is high but...
- \* You can use standard modules available in Quartus II library for most of the basic arithmetic operations
  - Some modules are technology dependent
  - Others are generic for any type of chip

Dr. Eduardo Castillo-Guerra

4

4



## Arithmetic with VHDL: Basic operators



- \* Involve the development of scripts that perform the arithmetic operations
- \* Scripts have to construct the logic functions required for the operation  
i.e. the addition of 1-bit is implemented with the equations:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY fulladd_L4_Slide7 IS
PORT(Cin , x, y  : IN  STD_LOGIC;
      s, Cout    : OUT STD_LOGIC);
END fulladd_L4_Slide7;

ARCHITECTURE logicFunc OF fulladd_L4_Slide7 IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y);
END logicFunc;
    
```

$$S_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Dr. Eduardo Castillo-Guerra

5

5




## Arithmetic with VHDL: Basic operators



- \* N-bit carry adder is the implemented instantiating this modules n-times
  - i.e. a 4-bit carry adders can be implemented as

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY adder4_L4_slide7 IS
PORT(
    Cin : IN STD_LOGIC ;
    x3, x2, x1, x0 : IN STD_LOGIC ;
    y3, y2, y1, y0 : IN STD_LOGIC ;
    s3, s2, s1, s0 : OUT STD_LOGIC := '0' ;
    Cout : OUT STD_LOGIC ;
END adder4_L4_slide7;
ARCHITECTURE Structure OF adder4_L4_slide7 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
    COMPONENT fulladd_L4_Slide7 IS
        PORT(Cin , x, y  : IN  STD_LOGIC;
              s, Cout    : OUT STD_LOGIC);
    END COMPONENT;
BEGIN
    stage0: fulladd_L4_Slide7 PORT MAP ( Cin, x0, y0, s0, c1 );
    stage1: fulladd_L4_Slide7 PORT MAP ( c1, x1, y1, s1, c2 );
    stage2: fulladd_L4_Slide7 PORT MAP ( c2, x2, y2, s2, c3 );
    stage3: fulladd_L4_Slide7 PORT MAP ( c3, x3, y3, s3, Cout );
END Structure;
    
```

 

A file must be saved with the same name:  
fulladd\_L4\_Slide7.vhd

Dr. Eduardo Castillo-Guerra

6

6



## Arithmetic with VHDL: Custom library



- \* Using PACKAGE to store a previous code in a custom library
  - `work.fulladd_package.all` contains the package definition of `fulladd_L4_Slide7.vhd`

```


LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE work.fulladd_package.all;

ENTITY fulladd_L18_Slide15 IS
    PORT (
        Cin      : IN    STD_LOGIC ;
        x3, x2, x1, x0 : IN    STD_LOGIC ;
        y3, y2, y1, y0 : IN    STD_LOGIC ;
        s3, s2, s1, s0 : OUT   STD_LOGIC ;
        Cout      : OUT   STD_LOGIC ;
    );
END fulladd_L18_Slide15;

ARCHITECTURE Structure OF fulladd_L18_Slide15 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
BEGIN
    stage0: fulladd_L4_Slide7 PORT MAP ( Cin, x0, y0, s0, c1 );
    stage1: fulladd_L4_Slide7 PORT MAP ( c1, x1, y1, s1, c2 );
    stage2: fulladd_L4_Slide7 PORT MAP ( c2, x2, y2, s2, c3 );
    stage3: fulladd_L4_Slide7 PORT MAP ( c3, x3, y3, s3, Cout );
END Structure;

```

 Indicates that the module `fulladd_L4_Slide7` is in this library.



7


7


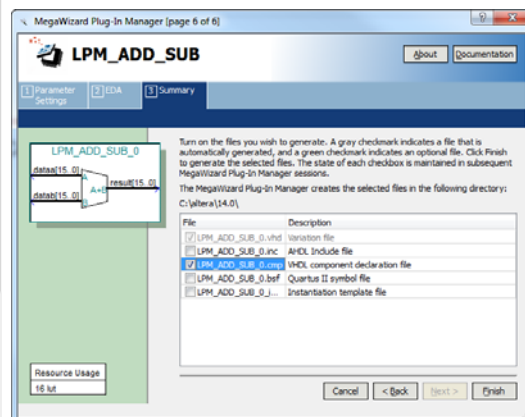
## Arithmetic with VHDL: QII LPM library



- \* You can generate arithmetic VHDL templates
  - `\Tools\IP Catalog`
  - Several configurable modules



8




8


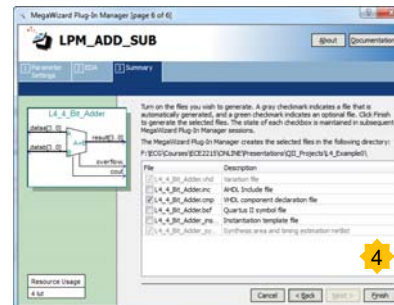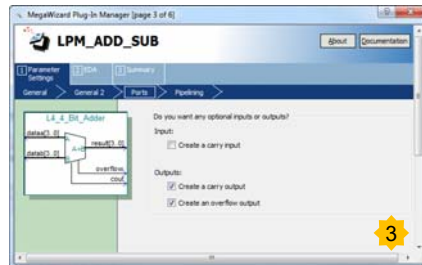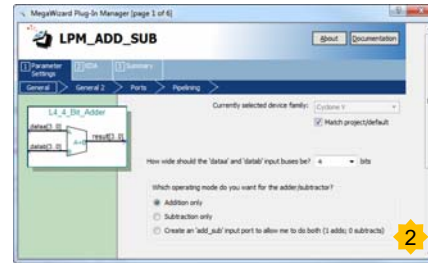
## Arithmetic with VHDL: QII LPM library



- \* Example 1 for the 4-bit carry adder
  - Creating the VHDL with LPM library



Dr. Eduardo Castillo-Guerra

9

9



## Arithmetic with VHDL: QII LPM library



- \* Files generated:
  - L4\_4\_Bit\_Adder.qip
  - L4\_4\_Bit\_Adder.vhd (fraction of the code below)

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

LIBRARY lpm;
USE lpm.all;

ENTITY L4_4_Bit_Adder IS
    PORT
    (
        dataa    : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        datab    : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        cout     : OUT STD_LOGIC;
        overflow  : OUT STD_LOGIC;
        result    : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)
    );
END L4_4_Bit_Adder;

ARCHITECTURE SYN OF L4_4_bit_adder IS

    SIGNAL sub_wire0 : STD_LOGIC;
    SIGNAL sub_wire1 : STD_LOGIC;
    SIGNAL sub_wire2 : STD_LOGIC_VECTOR (3 DOWNTO 0);
    
```

- \* Generated files must be added to the project and placed in the project root directory
- \* Use component to reuse the VHDL code generated

**You can generate circuits to multiply and divide in a similar way**

Dr. Eduardo Castillo-Guerra

10

10




## Arithmetic with VHDL: QII LPM library



### \* 4-bit adder implementation

```
1  -- Quartus II VHDL- Unsigned 4-bit carry adder
2  -- ECE2215 L4
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  entity L4_4_BIT_ADDER is
8  port (
9      a      : in STD_LOGIC_VECTOR (3 downto 0);
10     b      : in STD_LOGIC_VECTOR (3 downto 0);
11     carryout : out STD_LOGIC;
12     overflow : out STD_LOGIC;
13     sum      : out STD_LOGIC_VECTOR (3 downto 0)
14 );
15 end entity;
16
17 architecture rtl of L4_4_BIT_ADDER is
18     component FOUR_BIT_ADDER is
19     port
20     (
21         dataa : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
22         datab : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
23         cout  : OUT STD_LOGIC ;
24         overflow : OUT STD_LOGIC ;
25         result : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)
26     );
27     end component;
28
29 begin
30
31     I1: FOUR_BIT_ADDER PORT MAP (a, b, carryout, overflow, sum);
32
33 end rtl;
```

### Simulation results

 

Dr. Eduardo Castillo-Guerra

11



11


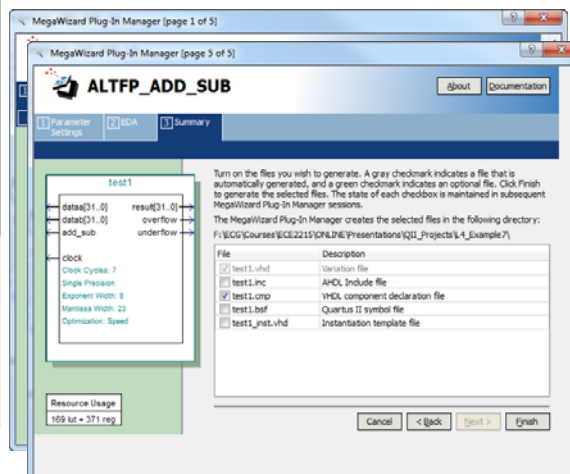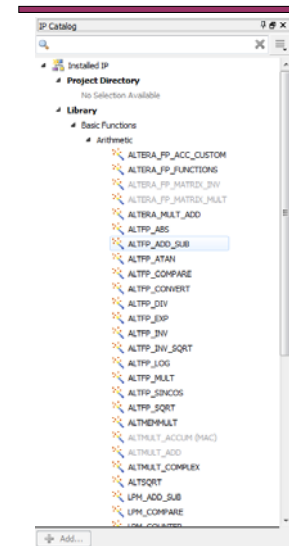
## Arithmetic with VHDL: QII ALTFP library



- \* Another VHDL library for floating point numbers
  - Several other functions from “\Tools\IP Catalog”
  - Addition/subtraction function



Dr. Eduardo Castillo-Guerra

12

12



## Arithmetic with VHDL: QII ALTFP library



\* Files generated:

- FP\_add\_sub\_function.qip,
- FP\_add\_sub\_function.vhd (fraction of the code below)

```

4860 LIBRARY ieee;
4861 USE ieee.std_logic_1164.all;
4862
4863 ENTITY FP_add_sub_function IS
4864     PORT
4865     (
4866         add_sub      : IN STD_LOGIC ;
4867         clock         : IN STD_LOGIC ;
4868         dataa         : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
4869         datab        : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
4870         overflow      : OUT STD_LOGIC ;
4871         result        : OUT STD_LOGIC_VECTOR (31 DOWNTO 0);
4872         underflow     : OUT STD_LOGIC ;
4873     );
4874 END FP_add_sub_function;
4875
4876 ARCHITECTURE RTL OF fp_add_sub_function IS
4877
4878     SIGNAL sub_wire0 : STD_LOGIC ;
4879     SIGNAL sub_wire1 : STD_LOGIC_VECTOR (31 DOWNTO 0);
4880     SIGNAL sub_wire2 : STD_LOGIC ;
4881

```

- \* Use component to reuse the VHDL code generated
- \* VHDL code generated has many different functions in the top part
  - scroll down to find main function
  - same name you provided earlier
- \* Use the function definition to declare the component and "port map" your local variables

Dr. Eduardo Castillo-Guerra

13

13



## Arithmetic with VHDL: QII ALTFP library



\* Single precision floating point adder/subtractor implementation

```

1  -- L4 Example 7- Floating Point add_sub with LPM library
2  -- ECE2215
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6
7  entity L4_FP_single_precision_add_sub is
8      port
9      (
10         add_subst    : IN STD_LOGIC ;
11         clk          : IN STD_LOGIC ;
12         numa         : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
13         numb         : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
14         overflow      : OUT STD_LOGIC ;
15         result        : OUT STD_LOGIC_VECTOR (31 DOWNTO 0);
16         undflow      : OUT STD_LOGIC ;
17     );
18 end entity;
19
20 architecture rtl of L4_FP_single_precision_add_sub is
21     COMPONENT FP_add_sub_function
22     PORT (
23         add_sub      : IN STD_LOGIC ;
24         clock         : IN STD_LOGIC ;
25         dataa         : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
26         datab        : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
27         overflow      : OUT STD_LOGIC ;
28         result        : OUT STD_LOGIC_VECTOR (31 DOWNTO 0);
29         underflow     : OUT STD_LOGIC ;
30     )
31 END COMPONENT;
32
33 begin
34     I1: FP_add_sub_function port map (add_subst,clk,numa,numb,overflow,result,undflow);
35
36 end rtl;

```

Dr. Eduardo Castillo-Guerra

14

14




## Arithmetic with VHDL: QII ALTFP library



- \* Single precision floating point adder/subtractor implementation

### Simulation results

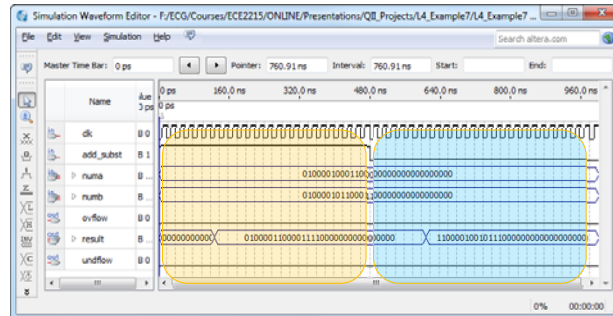

- \* Added  $44_{10}$  and  $99_{10}$  resulting  $143_{10}$ .
- \* Subtracted  $99_{10}$  from  $44_{10}$  resulting  $-55_{10}$ .
- \* A latency of 7 (7 clock cycle delay) to get result
- \* No overflow/underflow is generated

Dr. Eduardo Castillo-Guerra

15

15



## Arithmetic with VHDL: IEEE Numeric library



- \* This is the easiest approach
- \* Must include the library in your design as "use ieee.numeric\_std.all;"
- \* Includes operators for signed and unsigned arithmetic
  - Automatically select the right operation based on type of operands
  - Supported operators: '+', '-', '\*', '/', 'rem', 'mod', '\*\*', 'abs'
  - Other comparison and converting functions as seen in:  
[http://www.csee.umbc.edu/portal/help/VHDL/packages/numeric\\_std.vhd](http://www.csee.umbc.edu/portal/help/VHDL/packages/numeric_std.vhd)
  - Also support shifting operations basic gates with signed/unsigned types

Dr. Eduardo Castillo-Guerra

16

16





## Arithmetic with VHDL: IEEE Numeric library




### \* Example 1: 8-bit unsigned adder

```

1  -- L4 Example 1- Eight-bit unsigned adder
2  -- ECG 2016
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use ieee.numeric_std.all;
7
8  entity L4_8bit_unsigned_adder is
9      generic
10         (
11             DATA_WIDTH : natural := 8
12         );
13     port
14     (
15         a : in unsigned ((DATA_WIDTH-1) downto 0);
16         b : in unsigned ((DATA_WIDTH-1) downto 0);
17         result : out unsigned ((DATA_WIDTH-1) downto 0)
18     );
19 end entity;
20
21
22 architecture rtl of L4_8bit_unsigned_adder is
23 begin
24     result <= a + b;
25 end rtl;
26
27
28

```

 

\* All unsigned numbers are represented in hexadecimal as indicated by the H besides the variable's name

Dr. Eduardo Castillo-Guerra

17

17



## Arithmetic with VHDL: IEEE Numeric library




### \* Example 1: 8-bit signed adder

```

1  -- L4 Example- 8-bit Signed adder
2  -- ECG 2016
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use ieee.numeric_std.all;
7
8  entity L4_8bit_signed_adder is
9      generic
10         (
11             DATA_WIDTH : natural := 8
12         );
13     port
14     (
15         a : in signed ((DATA_WIDTH-1) downto 0);
16         b : in signed ((DATA_WIDTH-1) downto 0);
17         result : out signed ((DATA_WIDTH-1) downto 0)
18     );
19 end entity;
20
21
22 architecture rtl of L4_8bit_signed_adder is
23 begin
24     result <= a + b;
25 end rtl;
26
27
28

```

 

\* All signed numbers are represented in 2's complement

- 40-80ns → 00000001 (+ 1<sub>2s</sub>)
- 40-80ns → + 10000011 (- 125<sub>2s</sub>)
- result 10000100 (- 124<sub>2s</sub>)

Dr. Eduardo Castillo-Guerra

18

18



## Arithmetic with VHDL: IEEE Numeric library




### \* Example 1: 8-bit signed division

```

1  -- L4 Example 6- Signed Divider
2  -- Lecture 4 ECE2215 "/" and "rem" operators
3
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use ieee.numeric_std.all;
7
8  entity L4_8_bit_signed_div is
9  generic
10     (
11         DATA_WIDTH : natural := 8
12     );
13  port
14     (
15         a : in signed ((DATA_WIDTH-1) downto 0);
16         b : in signed ((DATA_WIDTH-1) downto 0);
17         cocient : out signed ((DATA_WIDTH-1) downto 0);
18         remainder : out signed ((DATA_WIDTH-1) downto 0)
19     );
20  end entity;
21
22  architecture rtl of L4_8_bit_signed_div is
23  begin
24
25
26         cocient <= a / b;
27         remainder <= a rem b;
28  end rtl;

```

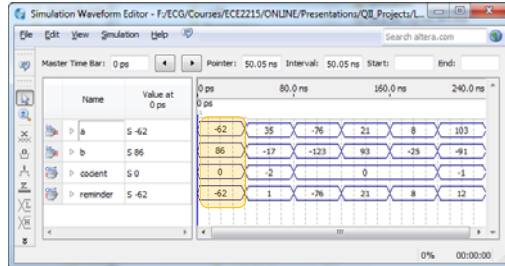

NOTE: Numbers were formatted as Signed decimal in the simulation window to facilitate the verification of the performed operations. i.e.

First set of testing numbers:

num1 →  $-62_{10} = 11000010_2$   
 num2 →  $+86_{10} = 01010110_2$   
 cocient →  $0_{10} = 11000010_2$   
 remainder →  $-62_{10} = 11000010_2$

Dr. Eduardo Castillo-Guerra

19

19



## Summary



- \* Arithmetic operators in VHDL
- \* Arithmetic with QII libraries
  - Signed and floating-point numbers
- \* Arithmetic with Numeric standard library
  - Signed and unsigned numbers
- \* Final exam recommendation
  - Bring code and Pin assignment from both boards
  - Bring any printed material you want
  - Will not have access to internet or online drives
  - Will be seated randomly
  - Practice bringing code compiled in other computers than the lab ones

Dr. Eduardo Castillo-Guerra

20

20