



# **ECE 2214**

## **Digital Logic Design**

### **L-30 FSM design examples**

**Fall 2022**



# Outline



- \* Design of a sequence detector with a Moore-type FSM
  - Schematic and VHDL implementation
- \* Design of a sequence detector FSM combining smaller Moore-type FSMs
  - Schematic
- \* Design of a sequence detector with a Mealy-type FSM
  - Schematic and VHDL implementation



# Summary of previous lecture


- \* FSM state minimization: Required when there are redundant states
  - Achieved with the ***partition minimization procedure***
- \* Hypothesis:
  - All the states in a given block are equivalent
  - States in different block are not equivalent
- \* Implementation
  - Start partitioning the blocks based on the k-successor method until no new group is generated
  - States in the same group are equivalent and can be minimized
  - Keep only one of them
- \* Analyzed an example
  - Method terminates when the next partition step do not reach any new group compared with the previous partition or...
  - Reach groups of only one variable



# Example 1

- \* Design a FSM that has an input  $w$  and an output  $z$  that...
  - Detects two consecutive previous values of the input in 00 or 11  $\rightarrow z = 1$
  - Otherwise,  $z = 0$ .
- \* **Solution:**
  - A similar problem to the example analyzed in previous lecture that detect a sequence of 11
  - Will follow the same approach to solve this problem
  - Will use a Moore machine because  $w$  depend on two consecutive previous stages
- \* Let C be the state that will be active when the sequence 00 occurs
- \* Let E be the state that will be active when the sequence 11 occurs

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	D	0
B	C	D	0
C	C	D	1
D	B	E	0
E	B	E	1

 



# Example 1

## \* Partition minimization procedure

$$P_1 = (ABCDE)$$

$$P_2 = (ABD)(CE)$$

- 0-sucessor of ABD → BCB  
→ B provides a 0-sucessor in a different group (C)
- 1-sucessor of ABD → DDE  
→ D provides a 1-sucessor in a different group (E)
- 0-sucessor of CE → CB → Both 0-sucessors are in different groups
- 1-sucessor of CE → DE → Both 1-sucessors are in different groups

$$P_3 = (A)(BD)(C)(E)$$

$$P_4 = (A)(B)(C)(D)(E)$$

- Since all variables appear in separate groups, the minimization procedure is stopped
- The optimum number of states is 5 and do not contain any redundancy
- \* Flip-flop selection & number: Since there are 5 states: 3 FFs are needed
  - Will use D FF

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	D	0
B	C	D	0
C	C	D	1
D	B	E	0
E	B	E	1



# Example 1

## \* State assignment

- The simplest state assignment is to follow the binary sequence starting from 000 and ending in 100 (101, 110, and 111 are used as don't care).

	Present state $y_3y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	000	001	011	0
B	001	010	011	0
C	010	010	011	1
D	011	001	100	0
E	100	001	100	1

	Present state	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
* Tr	A	B	D	0
	B	C	D	0
	C	C	D	1
	D	B	E	0
* Tr	E	B	E	1

$$z = y_3 + \overline{y_1}y_2$$

$y_3y_2$	$y_1w$			
	00	01	11	10
00	1	1	1	0
01	0	1	0	1
11	d	d	d	d
10	1	0	d	d

$y_3y_2$	$y_1w$			
	00	01	11	10
00	0	1	1	1
01	1	1	0	0
11	d	d	d	d
10	0	0	d	d

$y_3y_2$	$y_1w$			
	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	d	d	d	d
10	0	1	d	d

$y_3$	$y_2y_1$			
	00	01	11	10
0	0	0	0	1
1	1	d	d	d



# Example 1

- \* Next state equations seem to be unnecessarily complex
- \* This denotes that there should be a better state assignment scheme
- \* Note that state A is only reached at the beginning when the machine is started or reset. Therefore, it is better to assign codes starting with 100 to 111 to states BCDE

	Present state $y_3y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	000	100	110	0
B	100	101	110	0
C	101	101	110	1
D	110	100	111	0
E	111	100	111	1

- \* The equations of the next\_state are:

$$Y_1 = wy_2 + \bar{w}y_3\bar{y}_2$$

$$Y_2 = w$$

$$Y_3 = 1$$

- \* The output expression is:  $z = y_1$

$y_3y_2$	$y_1w$			
	00	01	11	10
00	0	0	d	d
01	d	d	d	d
11	0	1	1	0
10	1	0	0	1

$y_3y_2$	$y_1w$			
	00	01	11	10
00	0	1	d	d
01	d	d	d	d
11	0	1	1	0
10	0	1	1	0

$y_3y_2$	$y_1w$			
	00	01	11	10
00	1	1	d	d
01	d	d	d	d
11	1	1	1	1
10	1	1	1	1

$y_3$	$y_2y_1$			
	00	01	11	10
0	0	d	d	d
1	0	1	1	0


\* This is a better solution!



# Example 1



## \* Implementation

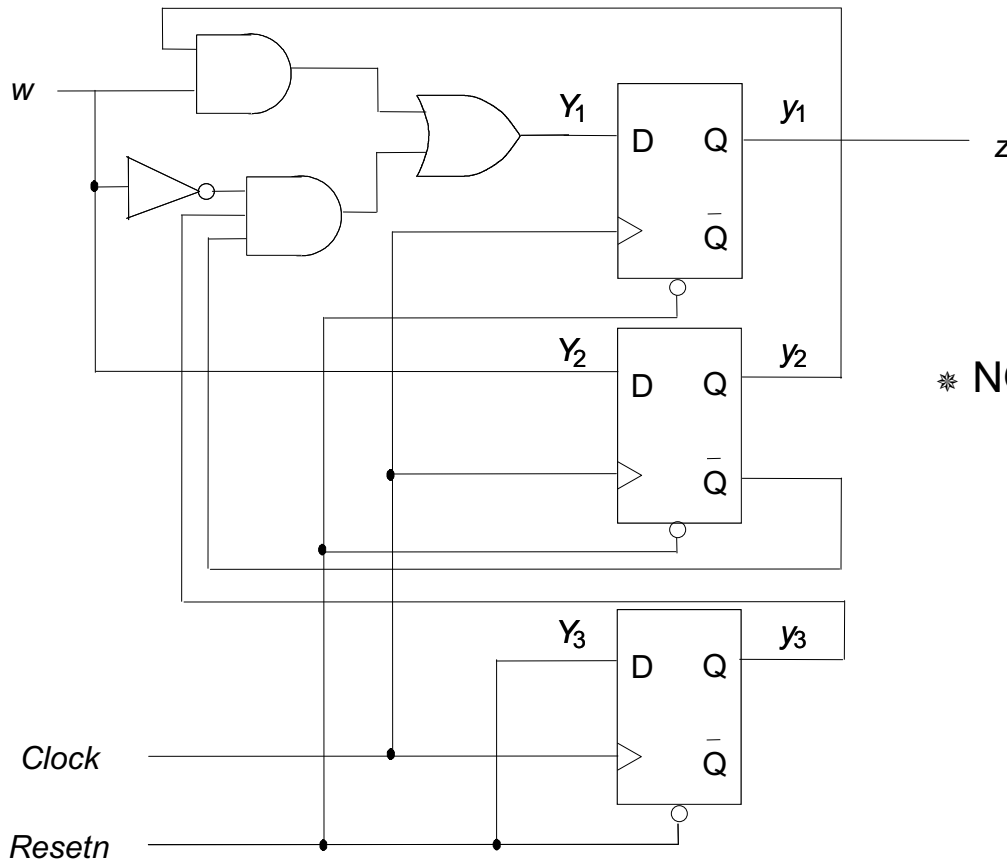

$$Y_1 = wy_2 + \overline{w}y_3\overline{y_2}$$

$$Y_2 = w$$

$$Y_3 = 1$$


$$z = y_1$$

## \* NOTE:

- $Y_3$  is 1 all the time since D FF will output the input D at the positive edge of the clock
- Can this help to further simplify provide?



## ✳ Implementation

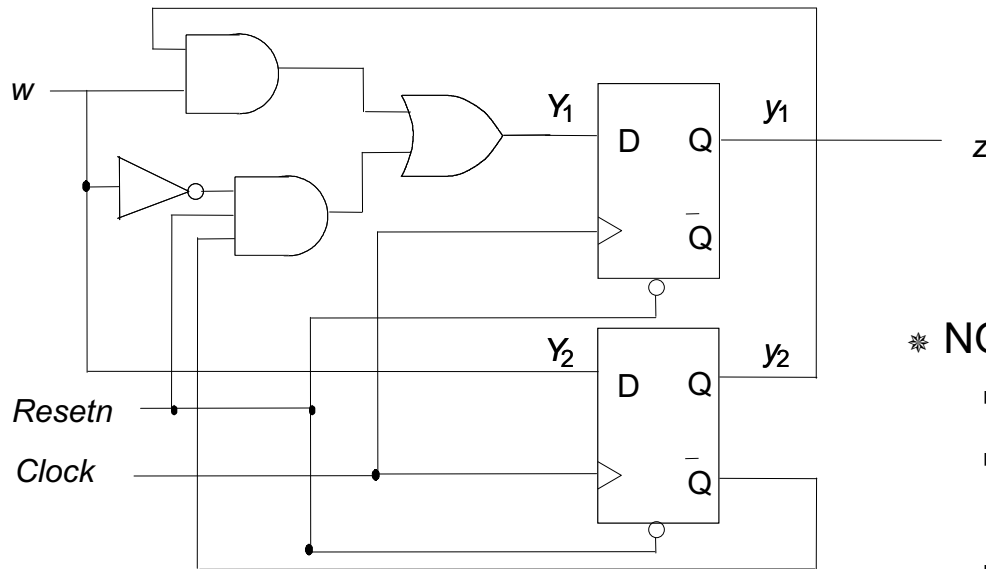

$$Y_1 = wy_2 + \overline{w}y_3\overline{y_2}$$

$$Y_2 = w$$

$$z = y_1$$

**\* NOTE:**

- Third FF can be eliminated
- Reset input can be connected directly to the AND gate
- This makes A a virtual state but ... will make the machine to operate asynchronously on the first clock cycle after reset
- This is more a practical solution since  $y_3$  doesn't change after the reset



# Example 1: VHDL implementation

## Automatic assignment



```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY simple IS
PORT ( Clock, Resetn, w : IN STD_LOGIC ;
      z : OUT STD_LOGIC ) ;
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
    TYPE State_type IS (A, B, C, D, E) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN
                        y <= B ;
                    ELSE
                        y <= D ;
                    END IF ;
            END CASE ;
        END IF ;
    END PROCESS ;
```

```
        WHEN B =>
            IF w = '0' THEN
                y <= C ;
            ELSE
                y <= D ;
            END IF ;
        WHEN C =>
            IF w = '0' THEN
                y <= C ;
            ELSE
                y <= D ;
            END IF ;
        WHEN D =>
            IF w = '0' THEN
                y <= B ;
            ELSE
                y <= E ;
            END IF ;
        WHEN E =>
            IF w = '0' THEN
                y <= B ;
            ELSE
                y <= E ;
            END IF ;
        END CASE ;
    END IF ;
END PROCESS ;
z <= '1' WHEN y = C OR y = E ELSE '0' ;
END Behavior ;
```

Present state	Next state		Output z
	w = 0	w = 1	
A	B	D	0
B	C	D	0
C	C	D	1
D	B	E	0
E	B	E	1



# Example 1: Alternative VHDL implementation

## Manual assignment



Present state	Next state		Output z
	w = 0	w = 1	
A	B	D	0
B	C	D	0
C	C	D	1
D	B	E	0
E	B	E	1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT ( Clock, Resetn, w : IN      STD_LOGIC ;
           z                  : OUT    STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(2 DOWNTO 0);
    CONSTANT A : STD_LOGIC_VECTOR(2 DOWNTO 0) := "000";
    CONSTANT B : STD_LOGIC_VECTOR(2 DOWNTO 0) := "100";
    CONSTANT C : STD_LOGIC_VECTOR(2 DOWNTO 0) := "101";
    CONSTANT D : STD_LOGIC_VECTOR(2 DOWNTO 0) := "110";
    CONSTANT E : STD_LOGIC_VECTOR(2 DOWNTO 0) := "111";
```

```
BEGIN
```

```
    PROCESS ( w, y_present )
```

```
    BEGIN
```

```
        CASE y_present IS
```

```
            WHEN A =>
```

```
                IF w = '0' THEN y_next <= B ;
                ELSE y_next <= D ;
                END IF ;
```

```
            WHEN B =>
```

```
                IF w = '0' THEN y_next <= C ;
                ELSE y_next <= D ;
                END IF ;
```

```
            WHEN C =>
```

```
                IF w = '0' THEN y_next <= C ;
                ELSE y_next <= D ;
                END IF ;
```

```
            WHEN D =>
```

```
                IF w = '0' THEN y_next <= B ;
                ELSE y_next <= E ;
                END IF ;
```

```
            WHEN E =>
```

```
                IF w = '0' THEN y_next <= B ;
                ELSE y_next <= E ;
                END IF ;
```

```
        END CASE ;
```

```
    END PROCESS ;
```

```
    PROCESS ( Clock, Resetn )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            y_present <= A ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

```
            y_present <= y_next ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
    z <= '1' WHEN y_present = C OR y_present = E ELSE '0' ;
```

```
END Behavior;
```



## Example 2


- \* Design the previous FSM combining two smaller FSMs such that one detects the 11 sequence and the other the sequence of 00
- \* **Solution:** The state table and circuit for the FSM that detects 11 were introduced in previous lecture

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2Y_1$	$Y_2Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$

The expressions for this FSM are:

$$Y_1 = w \quad z_{ONES} = y_2$$

$$Y_2 = wy_1$$

 



 
# Example 2



\* The state table for the FSM that detects 00 is:



Present state	Next state		Output $z_{zeros}$
	$w = 0$	$w = 1$	
D	E	D	0
E	F	D	0
F	F	D	1

Present state $y_4 y_3$	Next state		Output $z_{zeros}$
	$w = 0$	$w = 1$	
	$Y_4 Y_3$	$Y_4 Y_3$	
D	00	01	0
E	01	11	0
F	11	11	1
	10	dd	d

The expressions for this FSM are:

$$Y_3 = \bar{w}$$

$$Y_4 = \bar{w}y_3$$

$$z_{ZEROS} = y_4$$

$w \backslash y_4 y_3$	00	01	11	10
0	1	1	1	d
1	0	0	0	d

$w \backslash y_4 y_3$	00	01	11	10
0	0	1	1	d
1	0	0	0	d

$y_4 \backslash y_3$	0	1
0	0	0
1	d	1




## Example 2

- \* The circuit expression is:  $Z = Z_{ONES} + Z_{ZEROS}$

$$Y_3 = \overline{w}$$

$$Y_4 = \overline{w}y_3$$



$$Z_{ZEROS} = y_4$$

 

$$Y_1 = w$$

$$Y_2 = wy_1$$

$$Z_{ONES} = y_2$$

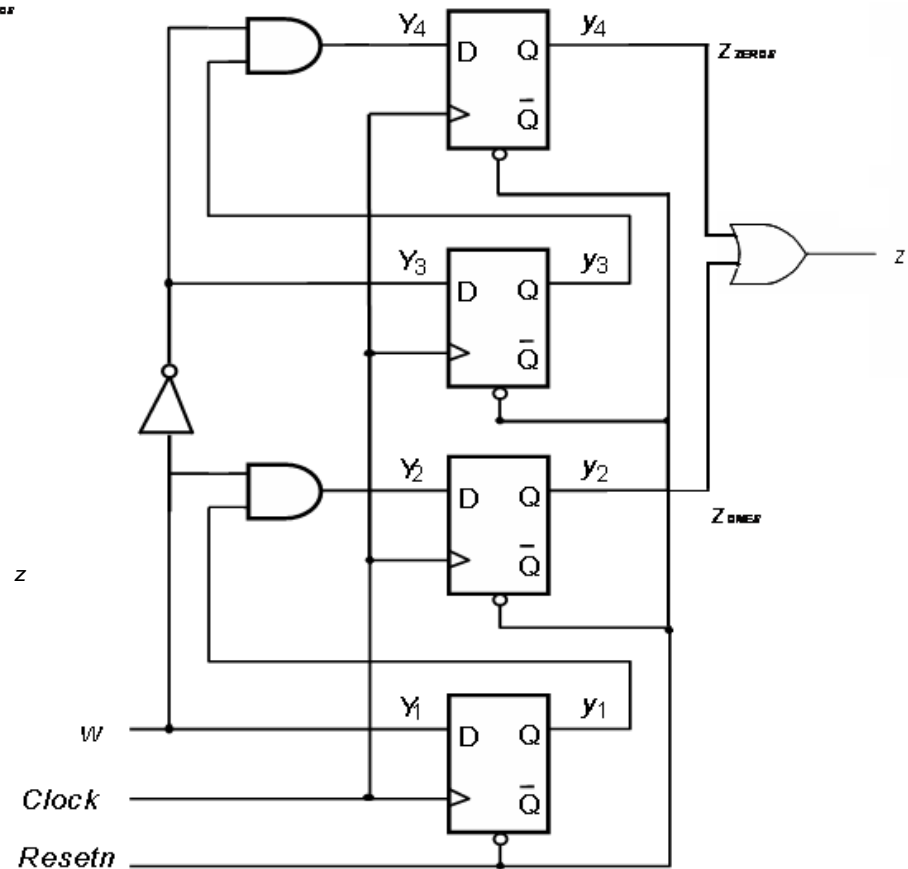 





 
## Example 3

- \* Design a Mealy-type FSM that detects the sequence 11 and 00 as in example 1 and write the VHDL code to implement the example in QUARTUS II
- \* **Solution:** The state diagram, state table and circuit for the Mealy FSM are:



Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	B	C	1	0
C	B	C	0	1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$z$	$z$
A	00	01	11	0	0
B	01	01	11	1	0
C	11	01	11	0	1





# Example 3

- \* This assignment leads to the next-state and output expressions:

$$Y_1 = 1$$

$$Y_2 = w$$

$$z = \overline{w}y_1\overline{y_2} + wy_2$$

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$z$	$z$
A	00	01	11	0	0
B	01	01	11	1	0
C	11	01	11	0	1

- \* Note that there are great savings using the input to determine the output
- \* Implementation changes from 3 FF in the Moore machine to 2 FF in the Mealy machine
- \* Logic cost is the same


		$y_2y_1$			
		00	01	11	10
$w$	0	1	1	1	d
	1	1	1	1	d

		$y_2y_1$			
		00	01	11	10
$w$	0	0	0	0	d
	1	1	1	1	d

		$y_2y_1$			
		00	01	11	10
$w$	0	0	1	0	d
	1	0	0	1	d



# Example 3 implementation

 

$$Y_1 = 1$$

$$Y_2 = w$$

$$z = \overline{w}y_1\overline{y_2} + wy_2$$



# Example 3: VHDL implementation

## Automatic assignment

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mealy IS
    PORT ( Clock, Resetn, w : IN  STD_LOGIC ;
          z                : OUT  STD_LOGIC ) ;
END mealy ;

```

```

ARCHITECTURE Behavior OF mealy IS
    TYPE State_type IS (A, B, C) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN y <= B ;
                    ELSE y <= C ;
                    END IF ;
                WHEN B =>

```

```

                    IF w = '0' THEN y <= B ;
                    ELSE y <= C ;
                    END IF ;
                WHEN C =>
                    IF w = '0' THEN y <= B ;
                    ELSE y <= C ;
                    END IF ;
            END CASE ;
        END IF ;
    END PROCESS ;

```

```

PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= NOT w ;
        WHEN C =>
            z <= w ;
    END CASE ;
END PROCESS ;
END Behavior ;

```

Present state	Next state		Output	
	w = 0	w = 1	w = 0	w = 1
y <sub>2</sub> y <sub>1</sub>	Y <sub>2</sub> Y <sub>1</sub>	Y <sub>2</sub> Y <sub>1</sub>	z	z
A 00	01	11	0	0
B 01	01	11	1	0
C 11	01	11	0	1



# Summary



- ✧ Example 1
  - Design of a sequence detector with a Moore-type FSM
  - Schematic and VHDL implementations
- ✧ Example 2
  - Design of a sequence detector FSM combining smaller Moore-type FSMs
- ✧ Example 3
  - Design of a sequence detector with a Mealy-type FSM
  - Schematic and VHDL implementations
- ✧ Recommended reading
  - Fundamentals of Digital Logic with VHDL Design 2nd Edition Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005. Chapter 8, pp. 496 – 535
- ✧ Next lecture
  - Design of counter using sequential circuit approach
    - Fundamentals of Digital Logic with VHDL Design 3/e, Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2009. Chapter 8, pp. 535 - 553