



# **ECE 2214**

## **Digital Logic Design**

### **L-22 Registers and Counters**

**Fall 2022**



# Outline






- \* Shift registers
- \* Counters and applications
- \* Asynchronous counter
- \* Synchronous counter
  
- \* Information
  - Q4 will take place tomorrow
  - L18 - L22



   
# Summary of previous lecture

- \* Introduced edge sensitive flip-flops
  - **Negative edge (D, T, JK)**
  - **Positive edge (D, T, JK)**



D	CL	Cr	Pr	$Q_n$	$\bar{Q}_n$
0	$\uparrow$	1	1	0	1
1	$\uparrow$	1	1	1	0
x	D	1	1	$Q_{n-1}$	$\bar{Q}_{n-1}$
x	D	1	1	$Q_{n-1}$	$\bar{Q}_{n-1}$
x	$\uparrow$	0	1	0	1
x	$\uparrow$	1	0	1	0

 




# Summary of previous lecture
 
## \* T flip-flop:


- Special type of flip-flop that toggles the outputs T



Graphical symbol


T	Q (t+1)
0	Q (t)
1	$\bar{Q} (t)$

Truth table

 
 
## \* J-K flip-flops :

- Synchronous device
- General type of flip-flop that can implement T and D flip-flops



CLK	J	K	$Q_n$	$\bar{Q}_n$
↑	0	0	$Q_{n-1}$	$\bar{Q}_{n-1}$
↑	0	1	0	1
↑	1	0	1	0
↑	1	1	$\bar{Q}_{n-1}$	$Q_{n-1}$
0	x	x	$Q_{n-1}$	$\bar{Q}_{n-1}$
1	x	x	$Q_{n-1}$	$\bar{Q}_{n-1}$

→ D-FF

→ T-FF



# Summary of previous lecture

- \* **Flip-flops in VHDL** : The implementation of flip-flops in VHDL are simple and can be implemented readily with conditional assignment
  - ▶ **Use IF statement to check the edge of clock variable**
  - ▶ **Use rising\_edge(clk) or falling\_edge(clock) to assign variables**


```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY flipflop IS  
    PORT ( D, Clock : IN    STD_LOGIC ;  
          Q          : OUT  STD_LOGIC) ;  
END flipflop ;  
  
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS ( Clock,D )  
    BEGIN  
        IF rising_edge(Clock) THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```

**Code for a D flip-flop**


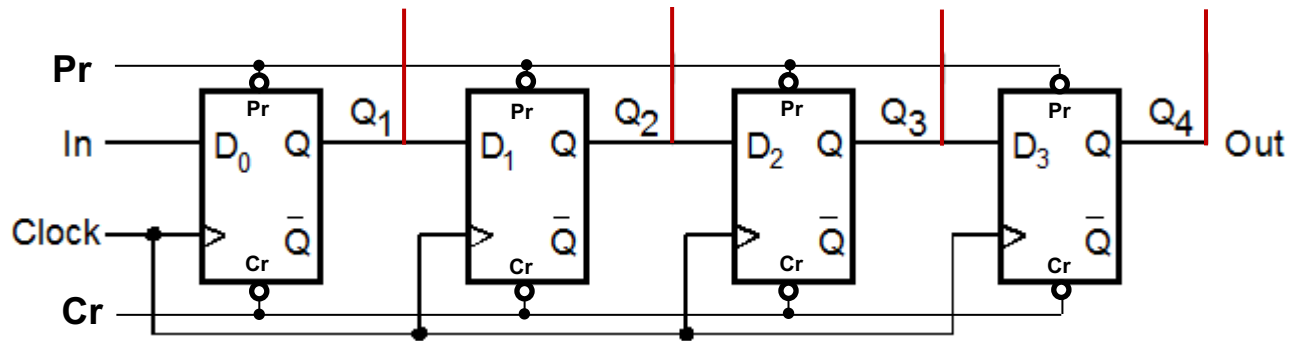
# Registers

- \* Registers are a set of **n** flip-flops used to store **n** bits of information
  - Each flip-flop stores one bit of data
  - Generally, the same clock drives all flip-flops




- Use **Pr**='0' inputs to set bits to "1"
- Use **Cr**='0' inputs to set bits to "0"
- Use **clock** to memorize bits in the flip-flops
- Input **In** used to enter data serially to the register
- Use **Cr** & **Pr** independently to load a particular 4-bit number


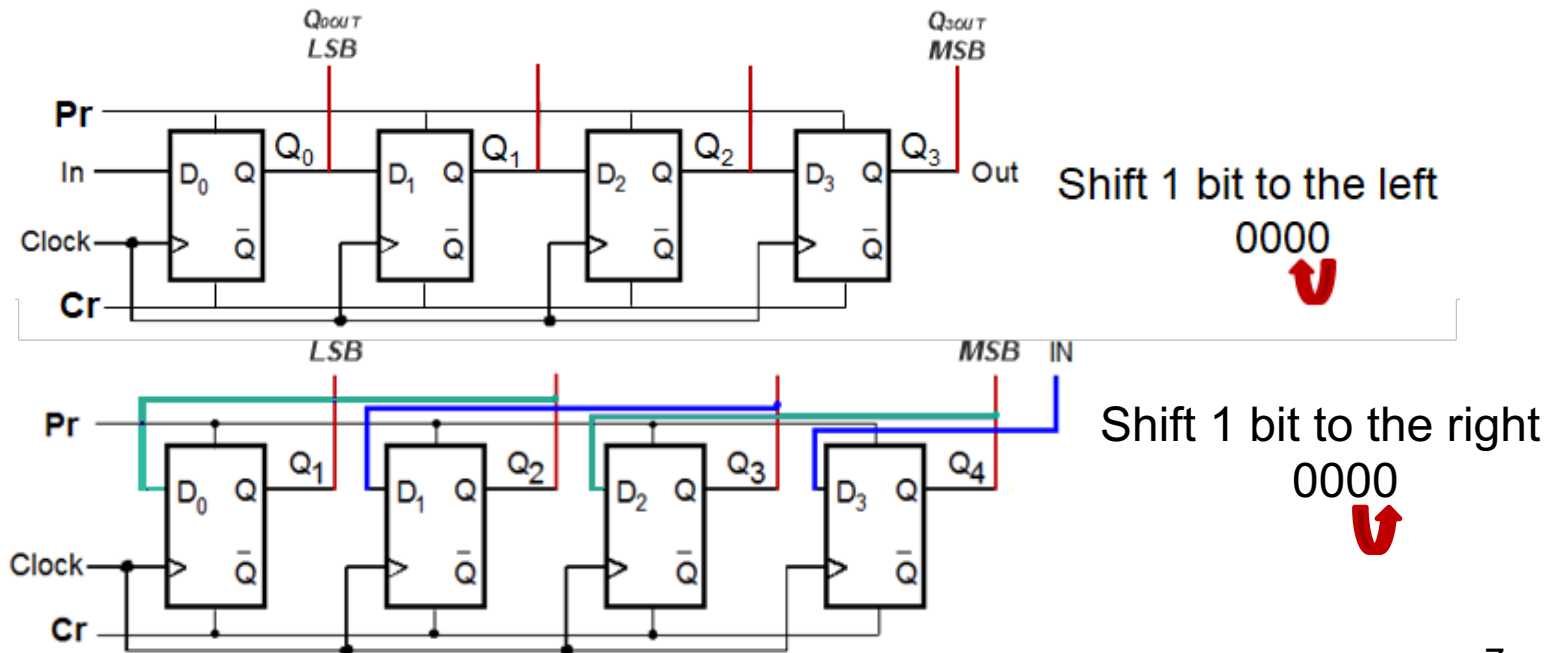
# Implementation of shift registers

- \* **Shift register:** a register that has the ability to shift stored bits based on a clock signal
  - Shift registers are very important for arithmetic operations, especially for multiplication and division.
  - For instance:
    - ▶ A binary number is multiplied by a power of 2 if it is shifted to the left, inserting zeros at the LSB
    - ▶ A binary number is divided by a power of 2 if it is shifted to the right inserting '0' at the MSB






# Registers
 
## \* Serial input/serial output register:

- Inputs are connected to output of previous FF to allow bit shifting
- Clocks are connected together to synchronize shifts
- $Q_3$  provides a serial output of the shifted bits



	In	$Q_0$	$Q_1$	$Q_2$	$Q_3 = \text{Out}$
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1


Circuit

**But... Computer need to access results at once  
(in parallel)**




 
# Serial input/parallel output shift register



Circuit

	In	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
t <sub>0</sub>	1	0	0	0	0
t <sub>1</sub>	0	1	0	0	0
t <sub>2</sub>	1	0	1	0	0
t <sub>3</sub>	1	1	0	1	0
t <sub>4</sub>	1	1	1	0	1
t <sub>5</sub>	0	1	1	1	0
t <sub>6</sub>	0	0	1	1	1
t <sub>7</sub>	0	0	0	1	1

## NOTE:


- \* Similar configuration to the serial version but outputs are obtained at once
- \* All clocks are connected together to synchronize shifts
- \* Computer can access values stored in the register in parallel


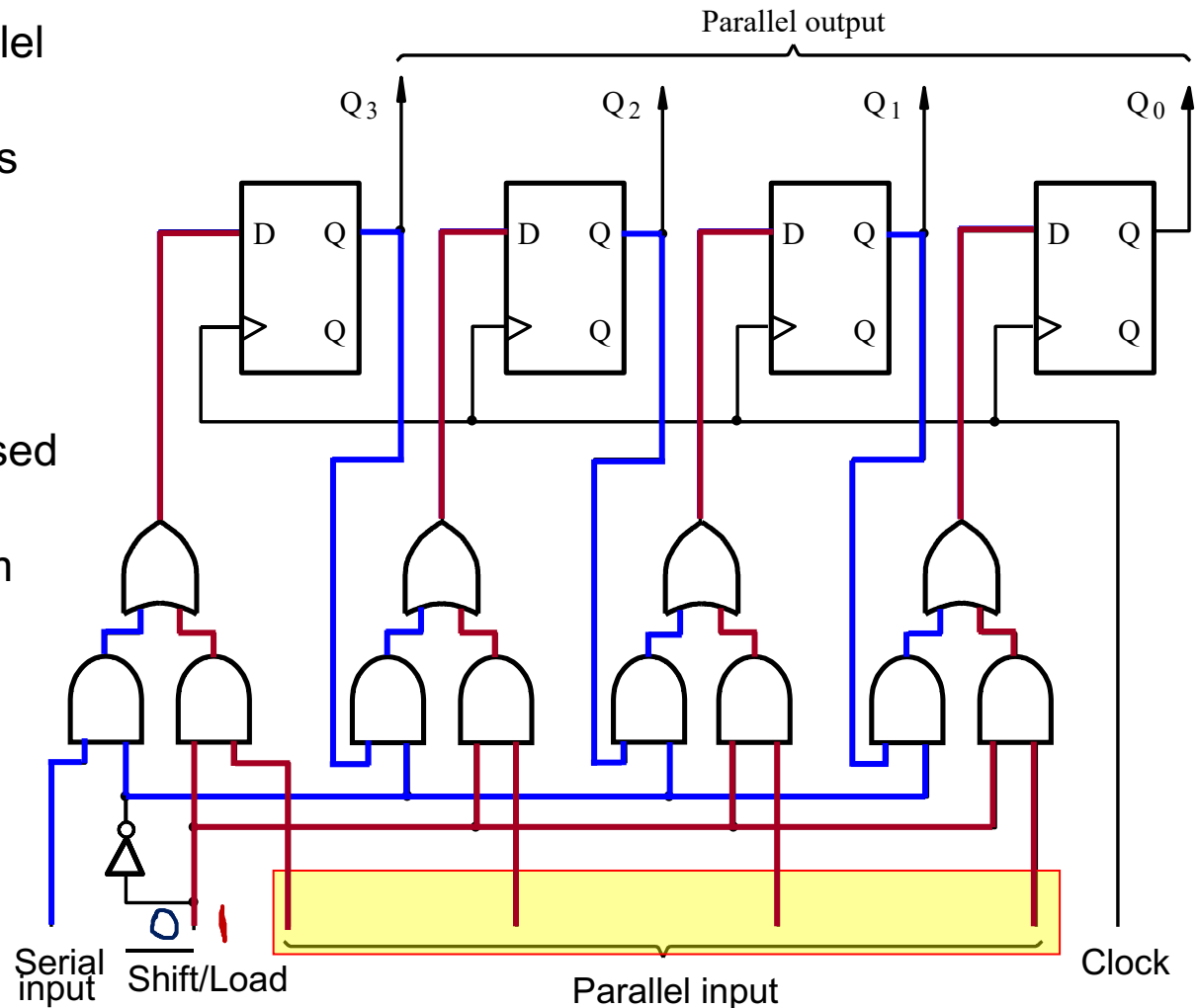
# Shift register with parallel load



- \* External circuit allows parallel load of external bits
- \* Parallel load used to set bits individually
- \* Control signal (Shift/Load) controls shift or load operations
- \* Output of each bit is accessed directly in parallel form
- \* A serial out is obtained from output  $Q_0$





# Counters


- ✧ Important to perform arithmetic operations such as addition and subtraction
  - Counters perform a special type of addition and subtraction used for counting: counts by one or a fixed magnitude
- ✧ Applications of counters
  - Many applications such as:
    - ▶ Count the number of occurrences of certain event
    - ▶ Generate timing signals to control different system tasks
    - ▶ Keep track of time elapsed between events, etc.
- ✧ Implementation of counters
  - Counters can be asynchronous and synchronous
  - The simplest ways of implementing a counter with F-Fs is:
    1. Using T flip-flops to toggle the output of the FF when the input variable meet the design condition
    2. Using D flip-flops to detect clock edge events



# Asynchronous counter

- \* Asynchronous counter: different clock signal for each bit (FF) so...
  - Each output do not change at the same time

- \* **Up-counter with T flip-flops**

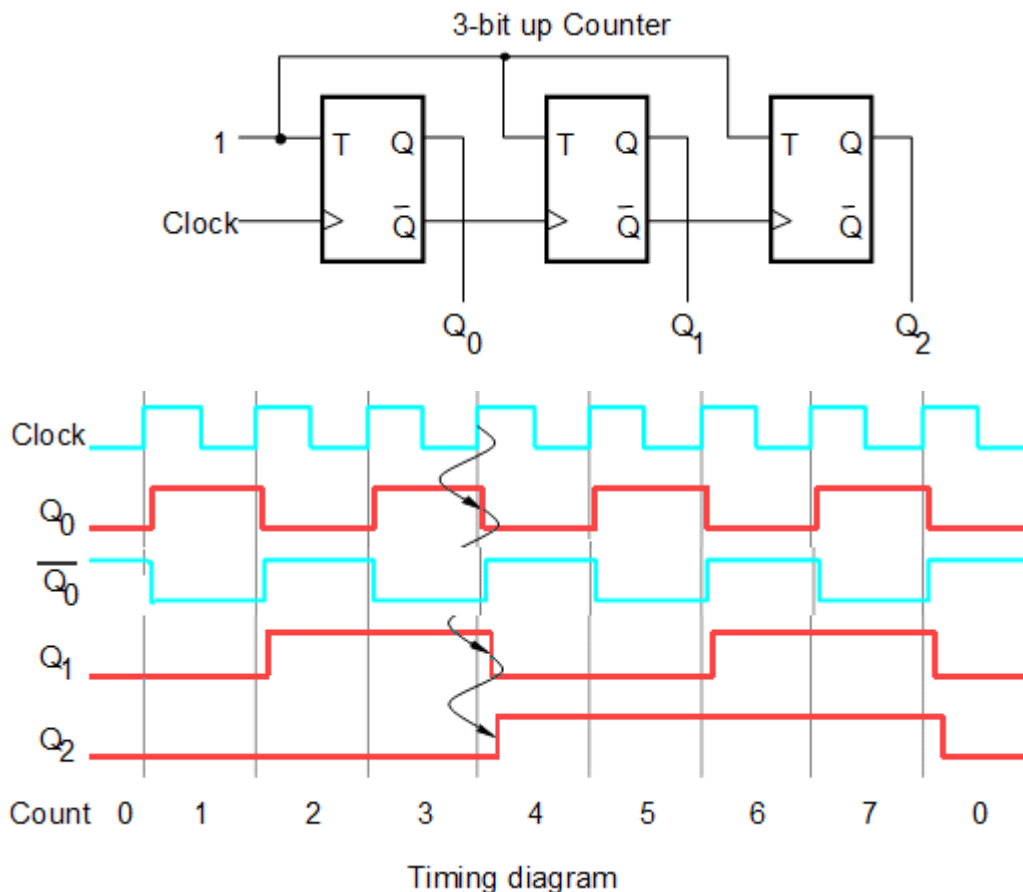


- \* Objective is to count the pulses of the input clock
- \* F-F are connected in cascade to provide consecutive bits
- \* T = 1 toggled FF output at CLK $\uparrow$   
That's why CLK<sub>1</sub> = clock
- \* CLK<sub>2</sub> = CLK<sub>3</sub> =  $\overline{Q_1}$  enable next-digit count event after previous digit counted the event and count up consecutively
- \* Q<sub>1</sub> and Q<sub>2</sub> will change with CLK $\downarrow$
- \* Q<sub>0</sub> is the LSB and Q<sub>2</sub> is the MSB
- \* Binary number is **Q<sub>2</sub>Q<sub>1</sub>Q<sub>0</sub>**
- \* Clock cascade introduces a propag. delay. **Drawback of asynchronous counting**



# Asynchronous counter

## \* Down-counter with T flip-flops

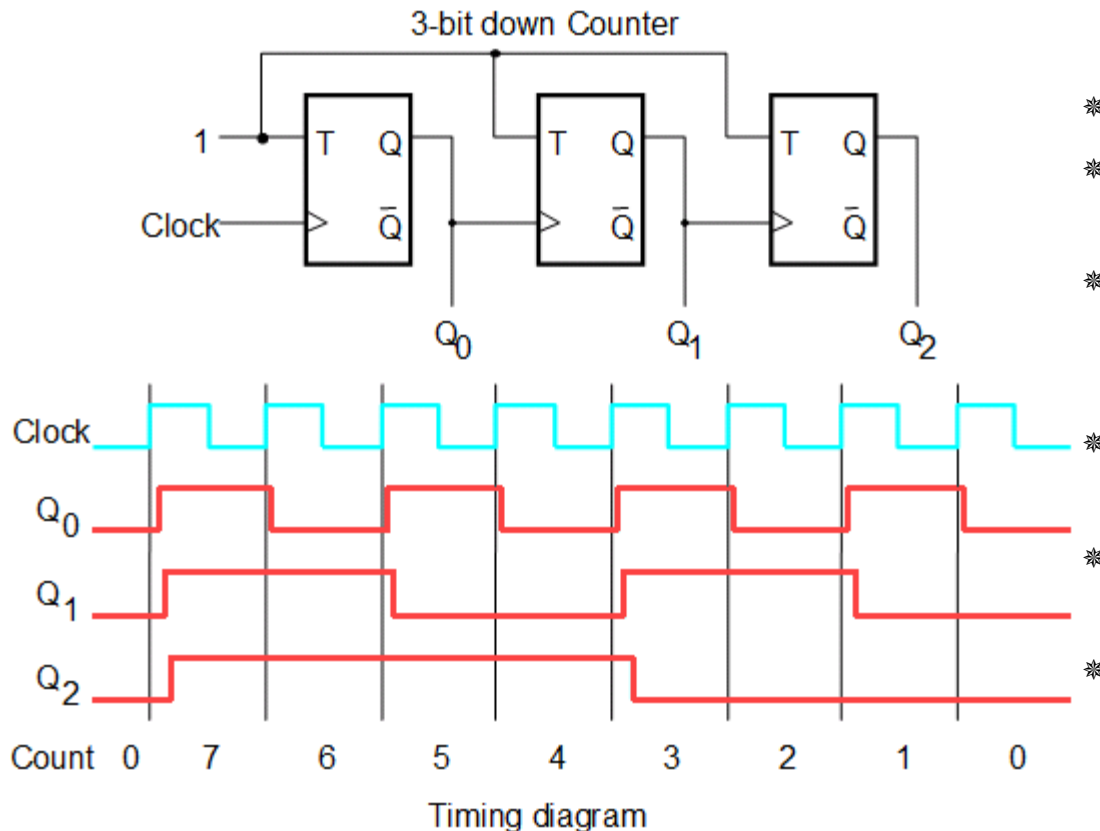

- \* Same configuration as the up counter
- \*  $CLK_2 = CLK_3 = Q$  now to enable down counting
- \*  $Q_1$  and  $Q_2$  will change with  $CLK \uparrow$  since are connected to Q of previous digit
- \* First state is "111" (max counting number)
- \* Suffer from the same drawback of asynchronous counting
- \* It is possible to combine this circuit with previous to form a up/down counter!

### Limitation:

- \* Delay increase with the number of bits
- \* Not suitable for strictly time-constrained applications



# Synchronous counter

- \* A more time-constrained implementation
- \* **Synchronous up-counter with T flip-flops:**
  - All clocks are set together to obtain synchronization
  - The inputs of the FFs have to be combined to obtain the counting sequence
- \* Derivation of counter equations :

Clock cycle	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q<sub>1</sub> changes

Q<sub>2</sub> changes

- \* The table represents the output of a 3-bit counter in the first 8 clock cycles

- \* Assume a starting state at '000':

- Q<sub>0</sub> changes in all states
- Q<sub>1</sub> will only change after Q<sub>0</sub> = 1
- Q<sub>2</sub> will only change after Q<sub>1</sub> = 1 and Q<sub>0</sub> = 1

- \* Implementing counter with T F-Fs require the following equations for the T inputs:



- $T_0 = 1$  (assumes initial T=1)
- $T_1 = Q_0$  (green column, out of FF<sub>0</sub>)
- $T_2 = Q_0Q_1$  (yellow column , out of FF<sub>1</sub>)

- \* Equations imply that all output of FFs have to be combined to reach counting sequence



# 4-bit counter implementation synchronous counter

4-bit synchronous up counter

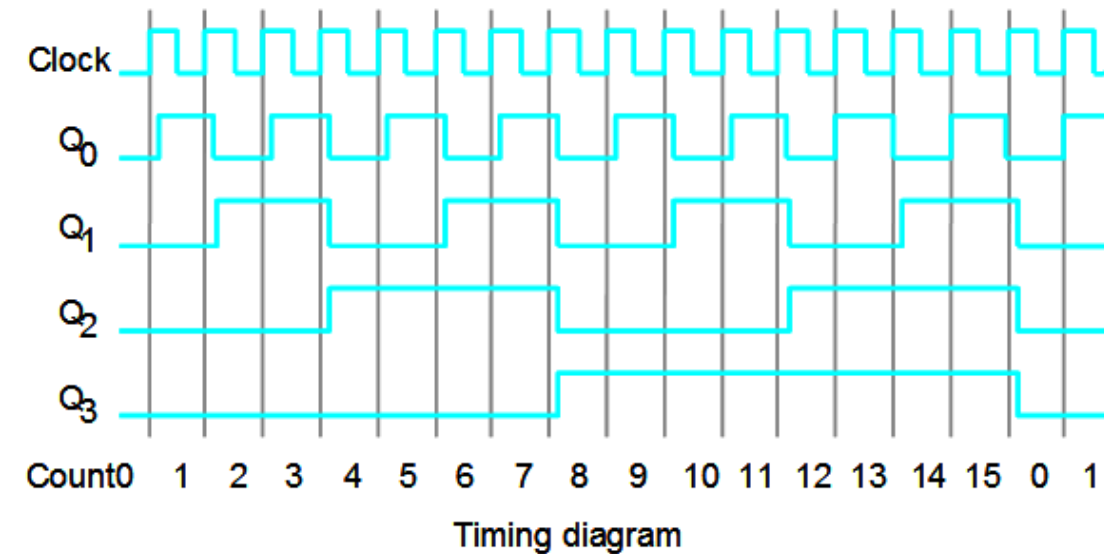 

- \* All clocks are connected to the same signal
- \* Note that:
  - $T_0 = 1$
  - $T_1 = Q_0$
  - $T_2 = Q_0 Q_1$
  - $T_3 = Q_0 Q_1 Q_2$
- \* The delay introduced at any stage is constant after the active edge of the clock signal
- \* The delays introduced do not depend on the number of bits but it is determined by the delay introduced by the F-F used

\* Notice that the output of a counter divide the frequency of the clock by a power of 2!



# Generalizing to n-bit up synchronous counters

- \* Generalizing for n-bit up counters:
  - A given F-F changes its states when all previous outputs are in state 1
  - Using T F-Fs to implement the counter, the following equations apply:

$$T_0 = 1 \text{ (assumes initial } T=1)$$

$$T_1 = Q_0$$

$$T_2 = Q_0Q_1$$

$$T_3 = Q_0Q_1Q_2$$

...

...

$$T_n = Q_0Q_1 \dots Q_{n-1}$$

- \* All F-Fs outputs have to be combined to enable the following bit






# 4-bit down counter implementation synchronous counter

- \* The complemented outputs of the FF used to enable the next bit

$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
...			
...			
0	0	0	1
0	0	0	0

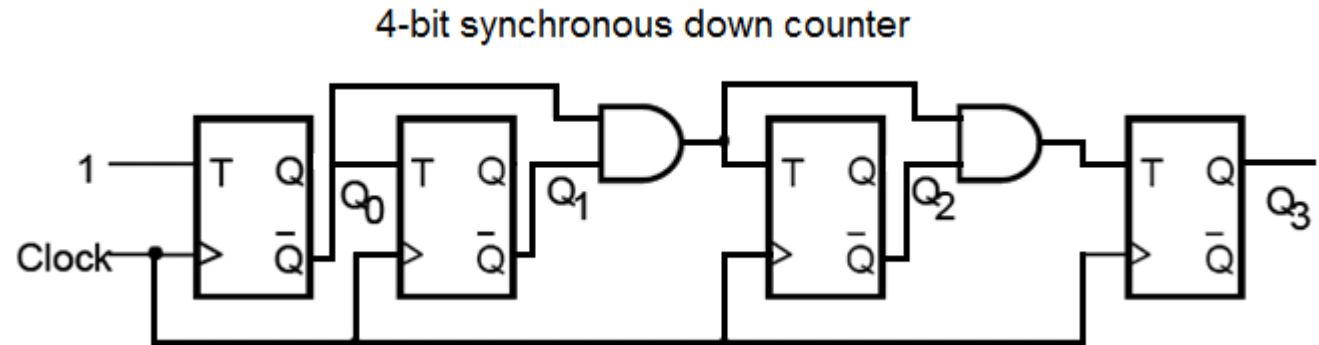

- \* Implementing down counter with T F-Fs require the following equations for the T inputs:

- $T_0 = 1$  (assumes initial  $T=1$ )
- $T_1 = \overline{Q_0}$
- $T_2 = \overline{Q_0} \overline{Q_1}$
- $T_3 = \overline{Q_0} \overline{Q_1} \overline{Q_2}$




# Enable and clear capabilities on counters



- \* **Enable:** Allows inhibiting the counter and holding the counting sequence
  - Easily achieved by setting the T inputs of the F-Fs to '0'
  - Freeze the counter at certain value until the data is read or the application performs a decision
  
- \* **Clear:** Allows resetting the counter where all bits will be set to 0
  - Achieved activating the clear terminal of all F-Fs
  - Allows changing the maximum counting value:
    - ▶ If additional logic is added to monitor the occurrence of a given number sequence
    - ▶ The logic activate the clear and resets counter outputs to 0


 
# Enable and clear capabilities on counters



- \* Enable = 0, set all T inputs to 0 and current counting sequence is frozen regardless any clock change
- \* Clear = 0, all Q outputs are set to 0 and current counting sequence is restarted
  - If FF has asynchronous reset
    - ▶ the change takes affect immediately
  - If FF has synchronous reset
    - ▶ the change won't take affect until next positive edge of the clock
- \* Preset = 0, preset to the maximum counting sequence



# Summary/references



- \* Shift registers
- \* Counters and applications
- \* Asynchronous and Synchronous counter
- \* Enable and reset features of counters
  
- \* Recommended exercises from the book
  1. Problems of pp. 473 of textbook (7.13-7.22)
  
- \* References
  - Fundamentals of Digital Logic with VHDL Design 2nd Edition Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005. Chapter 7, pp. 398-406.
  - Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 7, pp. 710-720, 727-752.
  
- \* Next Lecture
  - More on counters
  - Fundamentals of Digital Logic with VHDL Design 3/e, Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2009. Chapter 7, pp. 406-415.
  - Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 7, pp. 710-727.