



ECE 2214

Digital Logic Design

L-21 Flip-Flops

Fall 2022



Outline



- * Master-slave D flip-flops
- * Edge-triggered D flip-flops
- * Additional features of D flip-flops
- * T flip-flop
- * JK Flip flops
- * Flip-flops in VHDL





Summary of previous lecture

* Basic memory elements



▪ Basic SR latch:

  - ▶ Can store 1-bit of information but ...
- ▶ Limited by asynchronous outputs
- ▶ $S = R = 1$ can't occur otherwise $Q_a \neq Q_b$





▪ Gated SR latch:

  - ▶ Include a clock terminal to synchronize the output but...
- ▶ $S = R = 1$ can't occur otherwise $Q_a \neq Q_b$
- ▶ Asynchronous output while $CLK = 1$



▪ Gated D latch:

 
 
- ▶ Provide complemented outputs at any time
- ▶ $S = R = 1$ problem solved with a not gate
- ▶ Asynchronous out while $CLK = 1$ is not solved





Master-Slave D flip-flops

  
- * To solve the clock synchronism problem of the latches
 - Need to device circuits that ...
 - ▶ Can memorize digital information
 - ▶ Provide complemented outputs and...
 - ▶ Work synchronously with the CLK signal at all time
- * Master slave flip-flops were conceived to overcome this limitation!



- Two D latches governed by level edge resulting in edge control
 - ▶ Can be positive or negative clock edges
 - Figure corresponds to a Master-Slave active with negative clock edge




Master-Slave D flip-flops

 

Timing diagram

 From Fundamentals of Digital Logic with VHDL Design 2nd Ed. Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005



Circuit

- * Master latch changes when the clock changes to '1'
- * Slave changes when clock is '0'
- * The output of circuit changes with negative clock edge
 - The NOT gate guarantees edge synchronous behavior
 - Provide half of CLK to allow the output change

D	CLK	Q_n	\bar{Q}_n
0	↓	0	1
1	↓	1	0
x	0	Q_{n-1}	\bar{Q}_{n-1}
x	1	Q_{n-1}	\bar{Q}_{n-1}

Characteristic table


- * Flip-flops are **edge sensitive** rather than level sensitive




Positive edge D flip-flops



 - * Similar to a Master-slave flip-flop but with additional logic to ensure the output of the flip-flop will change with the positive edge of the clock signal
 - Show an optimized NAND gate implementation



Circuit

 

D	CLK	Q_n	\bar{Q}_n
0	↑	0	1
1	↑	1	0
x	0	Q_{n-1}	\bar{Q}_{n-1}
x	1	Q_{n-1}	\bar{Q}_{n-1}

Characteristic table


- * If $CLK = 0$, $P_1 = P_2 = 1$, $P_4 = \bar{D}$, & $P_3 = D$,
 - $Q_n = Q_{n-1}$ (output unchanged)
- * If $CLK = 1$, $P_1 = \bar{D}$ & $P_2 = D \rightarrow Q_n = D$

From Fundamentals of Digital Logic with VHDL Design 2nd Ed.
Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005

- * After CLK changes to 1, any change in D will not affect Q. Why?



Edge-triggered D flip-flops

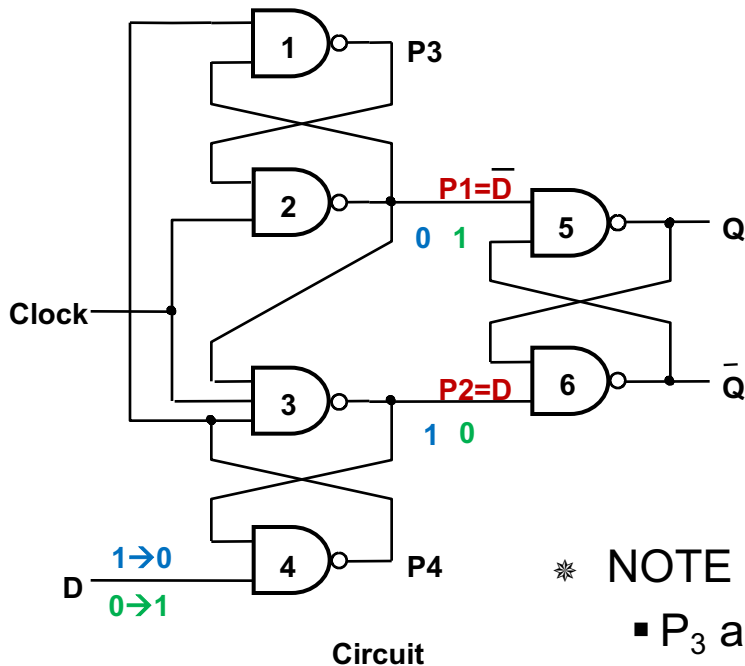

- * After CLK changes to 1, $P_1 = \overline{D}$ and $P_2 = D$
- * Any change in D will not affect Q because:
 - If before: $D = 1 \rightarrow P_1 = 0$ and $P_2 = 1$
 $D \rightarrow 0$ while $P_1 = 0$, $P_2 = 1$ regardless of D



* NOTE

- P_3 and P_4 must be stable when CLK \uparrow
- T_{SU} (stability of D value before CLK changes) of the F-F configuration is determined by the delay introduced by gates 4 and 1 when the signal propagates from input D to P_3
 - Longest data path
- T_H (hold time) is determined by gate 3
 - Once P_2 is stable, a change in D no longer matters



Level sensitive vs. edge-triggered D flip-flops

  * A comparison between the two types of flip-flops and the D latch...



From Fundamentals of Digital Logic with VHDL Design 2nd Ed. Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005

* Observation

- Any input change in D, is reflected in the output Q_a because it is level sensitive
- The output Q_b will reflect the state of input D with positive clock edge
- The output Q_c will reflect the state of input D with negative clock edge





Clear and preset features of D flip-flops

* The clear/preset input is used to set/reset the output of the flip-flop


- Activated preset \rightarrow sets $Q = 1$
- Activated clear \rightarrow reset $Q = 0$

  * Feature is important for many applications i.e. counters requiring resetting/presetting values



* Observation

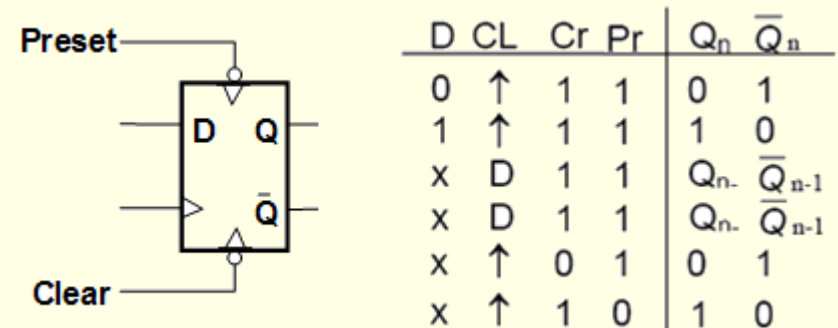
- Cr and Pr are active low
- Cr and Pr can't be active at the same time
- Cr and Pr are level sensitive
- Cr-Pr can be converted to edge sensitive






D flip-flops with clock enable

 - * Clock enable input allows preserving certain output state for a period of time determined by the enable pin



- * Observation

 
- The circuit does not control the clock
- D input is controlled instead
- $E_N = 1$, $Q_{N+1} = D$ with $CLK \uparrow$
- $E_N = 0$, $Q_{N+1} = Q_N$ when $CLK \uparrow$ regardless of the value of D
 - Achieved Q with a feedback of Q_N
- Both Cr and Pr inputs are applicable here (synchronous or asynchronous)





T flip-flop

 - * A special type of flip-flop that is also made by adding logic to a D flip-flop
- * It toggles the outputs with the active edge of the clock




* Observation


- Output Q is toggled with $T = 1$ and a positive edge of the clock
- Output Q does not change with $T = 0$
- Both Cr and Pr inputs are applicable here too (synchronous or asynchronous)

T	Q(t+1)
0	Q(t)
1	$\bar{Q}(t)$

Truth table

 

Graphical symbol

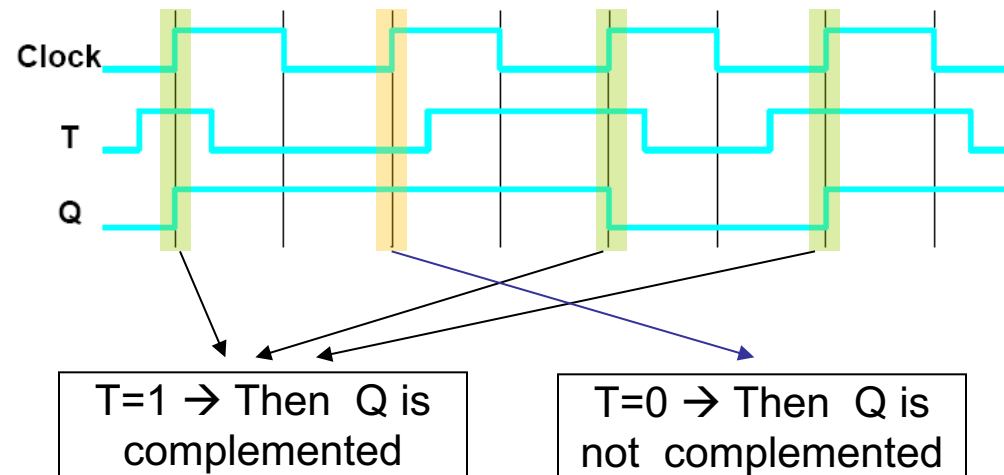



From Fundamentals of Digital Logic with VHDL Design 2nd Ed. Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005



J-K flip-flop



  - ✳ Similar to T F-F but they have 2 control inputs J and K
- ✳ Combine the characteristics of the D and T F-Fs
- ✳ Edge sensitive device
- ✳ The equation describing D is: $D = J\bar{Q} + \bar{K}Q$



CLK	J	K	Q_n	\bar{Q}_n
↑	0	0	Q_{n-1}	\bar{Q}_{n-1}
↑	0	1	0	1
↑	1	0	1	0
↑	1	1	\bar{Q}_{n-1}	Q_{n-1}
0	x	x	Q_{n-1}	\bar{Q}_{n-1}
1	x	x	Q_{n-1}	\bar{Q}_{n-1}

→ D-FF

→ T-FF

- ✳ J-K F-F is versatile
 - ✳ Behaves like a D-FF when $J = D$ and $K = \bar{D}$
 - ✳ Behaves as a T F-F if $J=K=T$
 - It toggles the output in every CLK ↑




Latches and flip-flops in VHDL



- * VHDL implementation of Latches and F-F is simple
- * Can be implemented with sequential assignment

- **IF** and **Case** statements

 - * Examples of implementations:
- * Example 1: Code for a gated D latch



- * Notice that when Clock = 1 , any change in D will be reflected in Q
- * When clock = 0, Q will not change with a change in D

From Fundamentals of Digital Logic with VHDL Design 2nd Ed. Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY GDlatch IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q          : OUT  STD_LOGIC ) ;
END GDlatch ;
```

```
ARCHITECTURE Behavior OF GDlatch IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



Flip-flops in VHDL


* EXAMPLE 2: Code for a D flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN     STD_LOGIC ;
          Q         : OUT    STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Clock, D )
    BEGIN
        IF rising_edge( Clock) THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

 From Fundamentals of Digital Logic with VHDL
Design 2nd Ed. Stephen Brown, Zvonko
Vranesic; McGraw-Hill, 2005



- * Rising_edge can also be implemented with (Clock'EVENT AND Clock = '1')
- * Clock'EVENT is a VHDL construct called attribute
- * It is a property of the object SIGNAL (Clock in this case)
- * Clock'EVENT refers to any change in clock signal
- * Clock = '1' refers to positive clock edge
- * Falling_edge(Clock) or Clock'EVENT AND Clock = '0' refers to negative clock edge




Flip-flops in VHDL



 * EXAMPLE 3: Code for a T flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY flipflop IS
    PORT ( T, Clock : IN    STD_LOGIC ;
          Q, Qn    : OUT  STD_LOGIC) ;
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
    SIGNAL Qt :   STD_LOGIC;
BEGIN
    PROCESS ( Clock,T )
    BEGIN
        IF rising_edge(Clock) AND T='1' THEN
            Qt <= NOT(Qt) ;
        END IF ;
    END PROCESS ;
    Q <= Qt;
    Qn<=NOT(Qt);
END Behavior ;
```



From Fundamentals of Digital Logic with VHDL Design 2nd
Ed. Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005




Flip-flops in VHDL

* EXAMPLE 4: Code for a T flip-flop with synchronous clear and preset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY Tflipflop IS
    PORT (T, Cr,Pr,clk : IN    STD_LOGIC ;
          Q, Qn      : OUT  STD_LOGIC) ;
END Tflipflop ;
ARCHITECTURE Behavior OF Tflipflop IS
    SIGNAL Qt :  STD_LOGIC;
BEGIN
    PROCESS ( clk,T, Cr, Pr )
    BEGIN
        IF rising_edge(clk) THEN
            IF (Cr XOR Pr) = '1' THEN  Qt <= Cr;
            ELSE Qt <= Qt XOR T;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Qt; Qn<=NOT(Qt);
END Behavior ;
```

T	clk	Cr	Pr	Q_n	\bar{Q}_n
0	↑	1	1	Q_{n-1}	\bar{Q}_{n-1}
1	↑	1	1	\bar{Q}_{n-1}	Q_{n-1}
x	0	1	1	Q_{n-1}	\bar{Q}_{n-1}
x	1	1	1	Q_{n-1}	\bar{Q}_{n-1}
x	↑	0	1	0	1
x	↑	1	0	1	0

 



Summary

- ✧ Introduced
 - Master-slave and Edge-triggered D flip-flops
 - Additional features of D flip-flops: ***Clear***, ***Preset*** and ***Enable***
 - T and J-K flip-flops
- ✧ Revised VHDL implementation of flip-flops
- ✧ Recommended study from the textbook
 1. Study solved problems 7.13 & 7.14
 2. Answer problems 7.1- 7.12



Reference

- ✱ Fundamentals of Digital Logic with VHDL Design 2nd Edition Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2005. Chapter 7, pp. 391-400
- ✱ Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 7, pp. 532-542

- ✱ Next lecture:
 - Registers
 - ▶ Fundamentals of Digital Logic with VHDL Design 3/e, Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2009. Chapter 7, pp. 398-406
 - ▶ Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 7, pp. 710-720, 727-752